

# POTENTIOMETERS AND HOW TO USE THEM

Professor Jon E. Froehlich

@jonfroehlich | [jonf@cs.uw.edu](mailto:jonf@cs.uw.edu)



**W** PAUL G. ALLEN SCHOOL  
OF COMPUTER SCIENCE & ENGINEERING

UNIVERSITY of  
WASHINGTON

## VARIABLE RESISTORS

# WHAT IS A POTENTIOMETER?




American-Style Symbol



International-Style Symbol



Resistive material


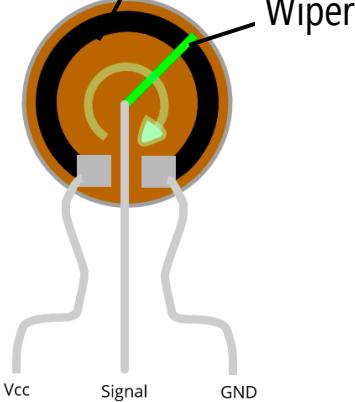


A **three-terminal resistor** with a sliding or rotating contact that forms an adjustable voltage divider

If only two terminals are used, the potentiometer acts as a **rheostat** or a two-terminal variable resistor


## POTENTIOMETERS
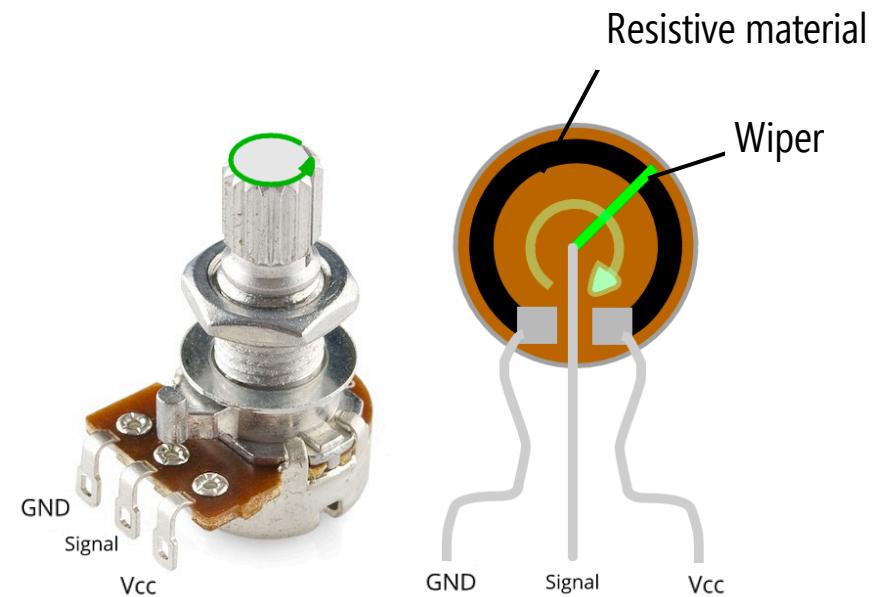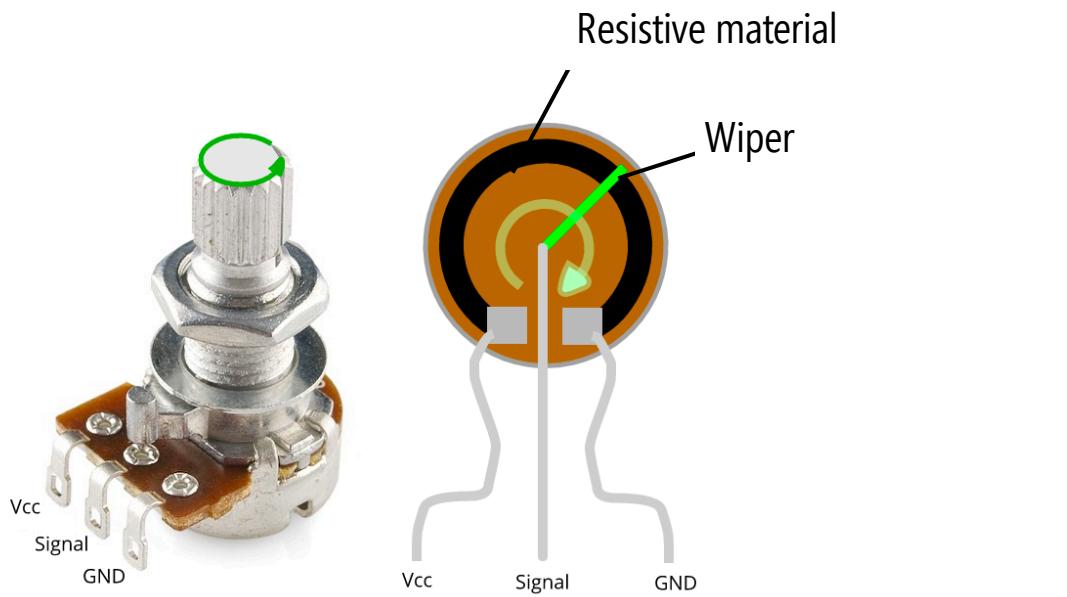
# POTENTIOMETERS CAN BE HOOKED UP IN EITHER ORIENTATION




POTENTIOMETERS

# DEMO OF LO-FI POTENTIOMETER

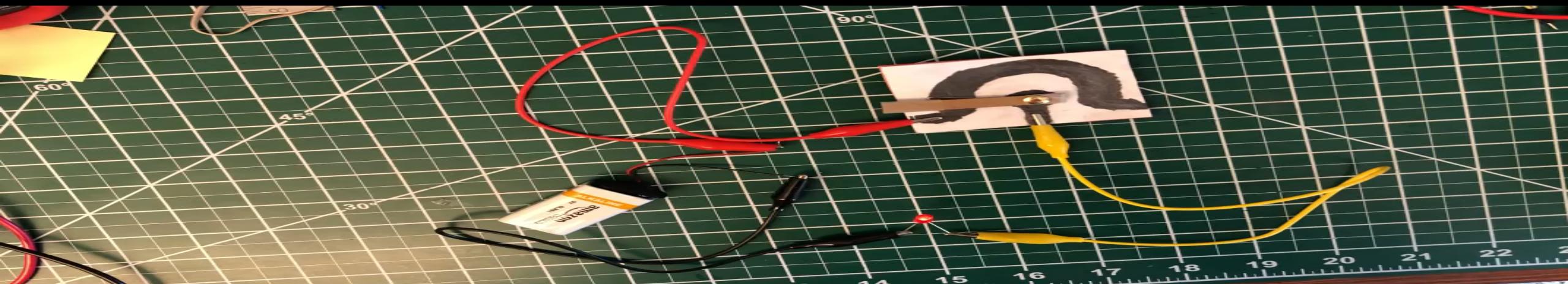

Video by Jon Froehlich

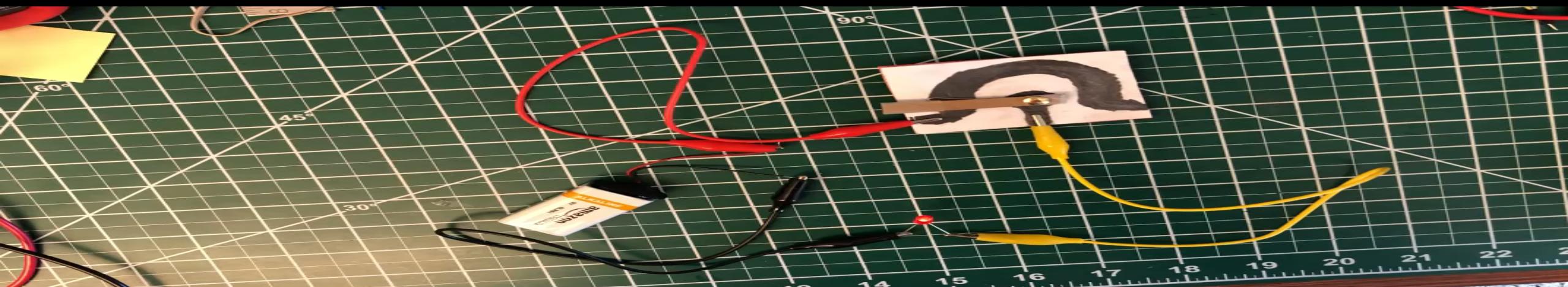


POTENTIOMETERS

# INSIDE A POTENTIOMETER




**CTS EP086 500k**

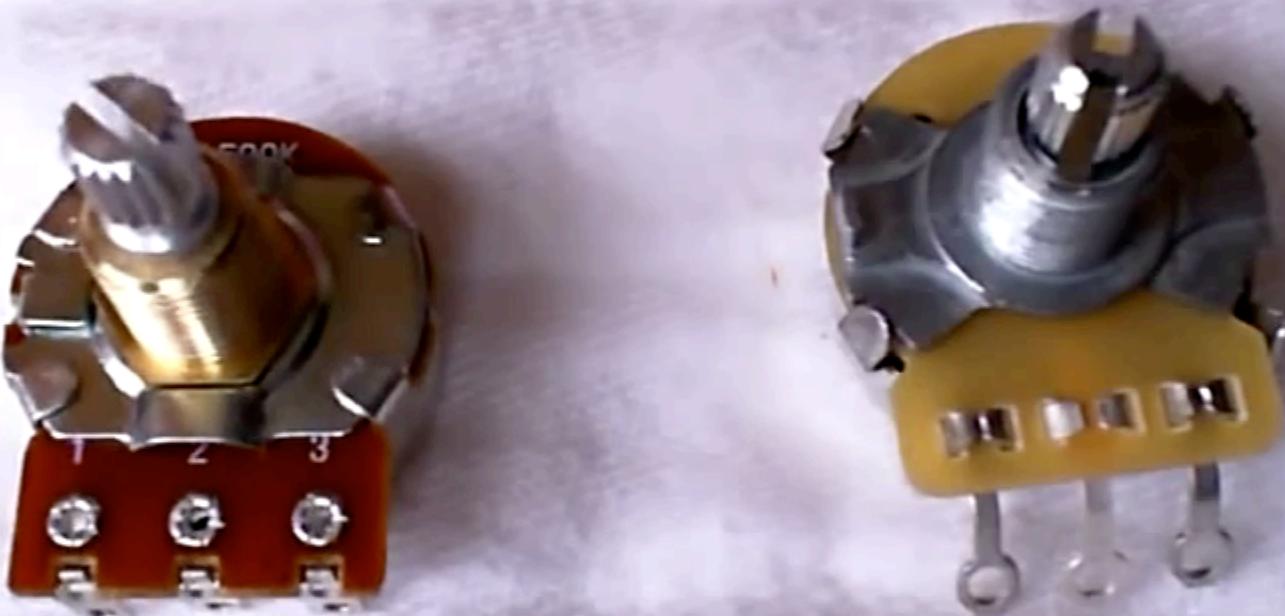

**CTS EP086 500k**



POTENTIOMETER

# RESISTOR VS. POTENTIOMETER

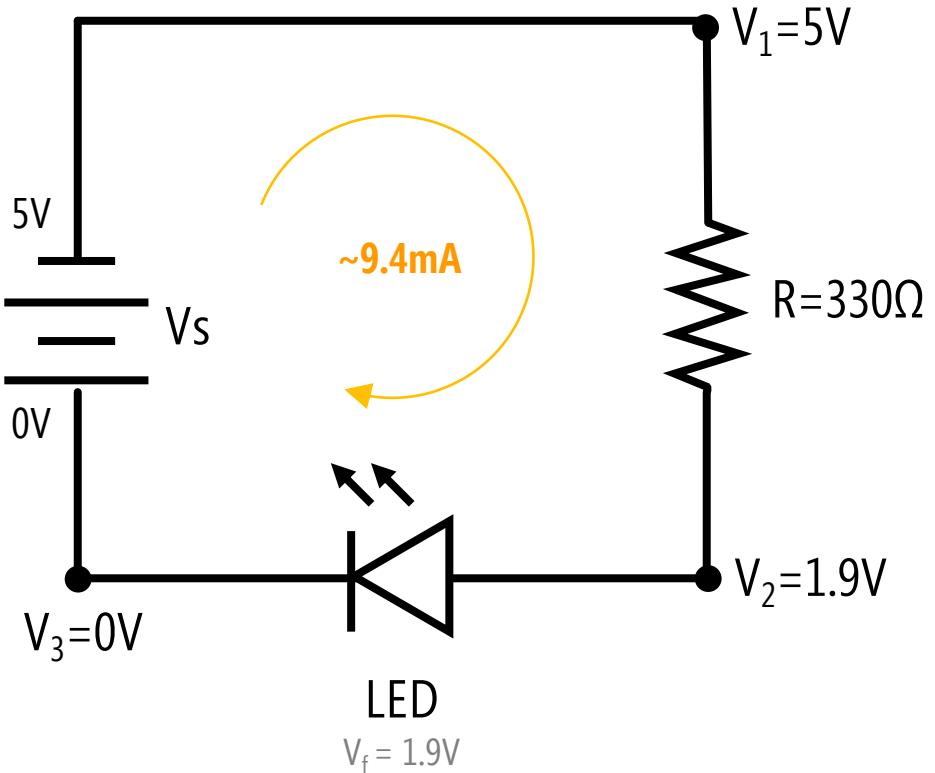



POTENTIOMETER

# RESISTOR VS. POTENTIOMETER

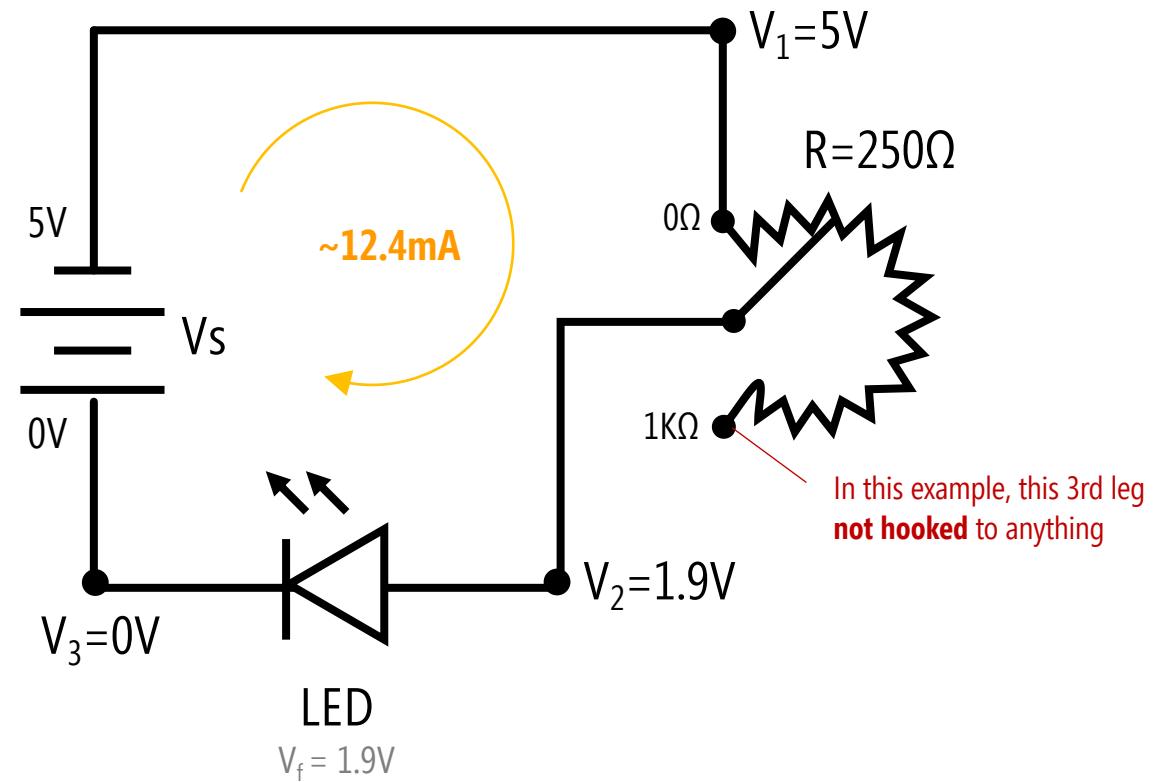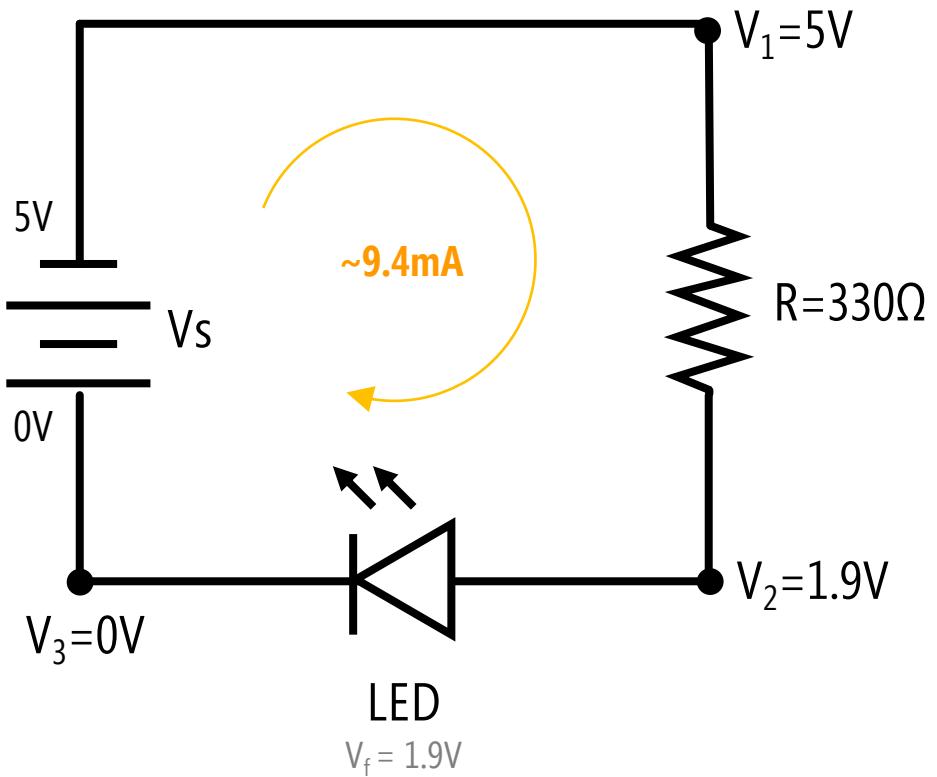



POTENTIOMETER

# RESISTOR VS. POTENTIOMETER

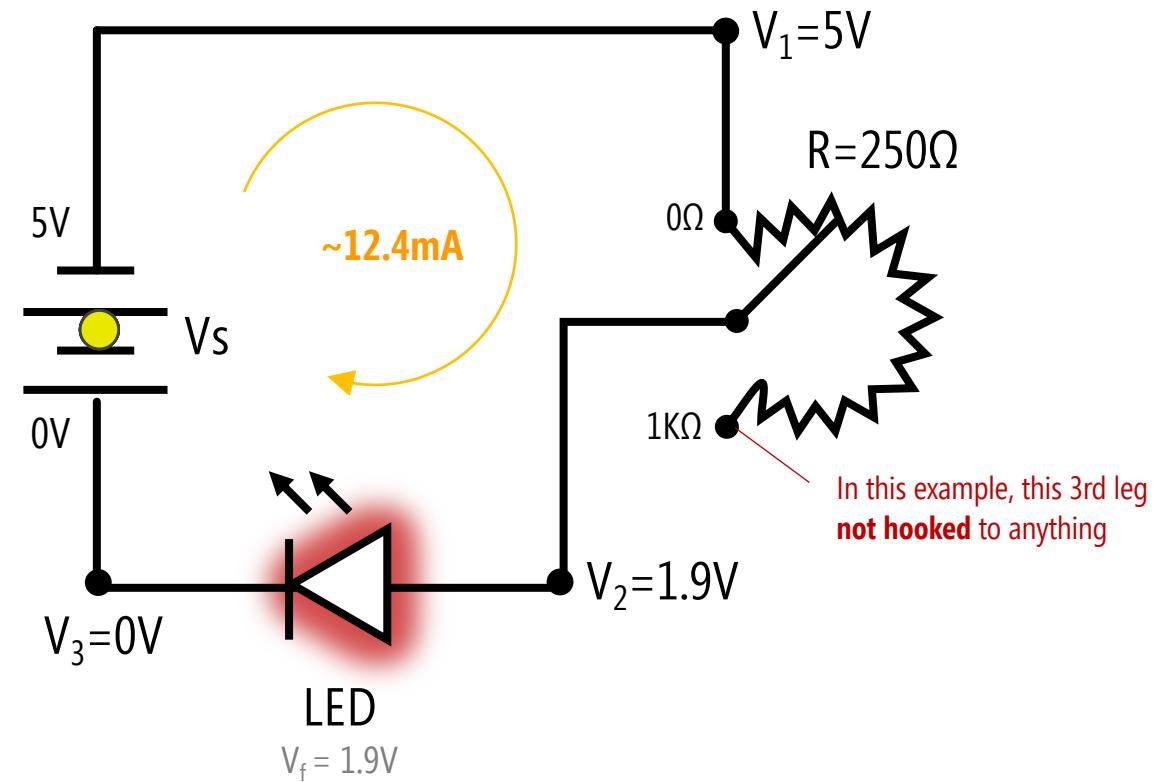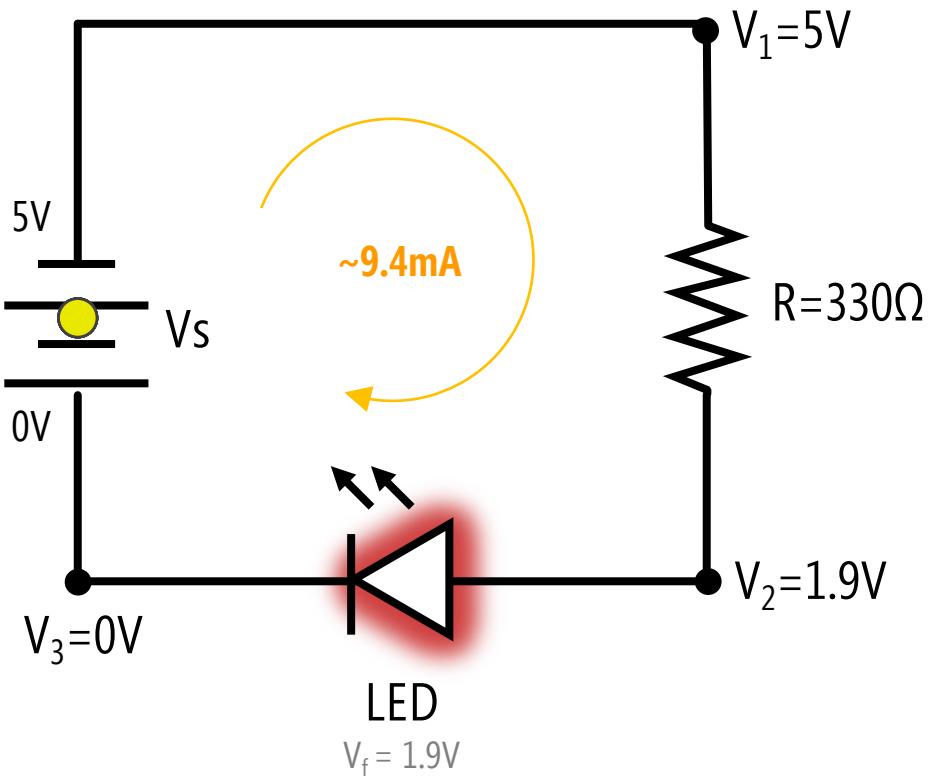



## POTENTIOMETER

# POTENTIOMETER EXAMPLES

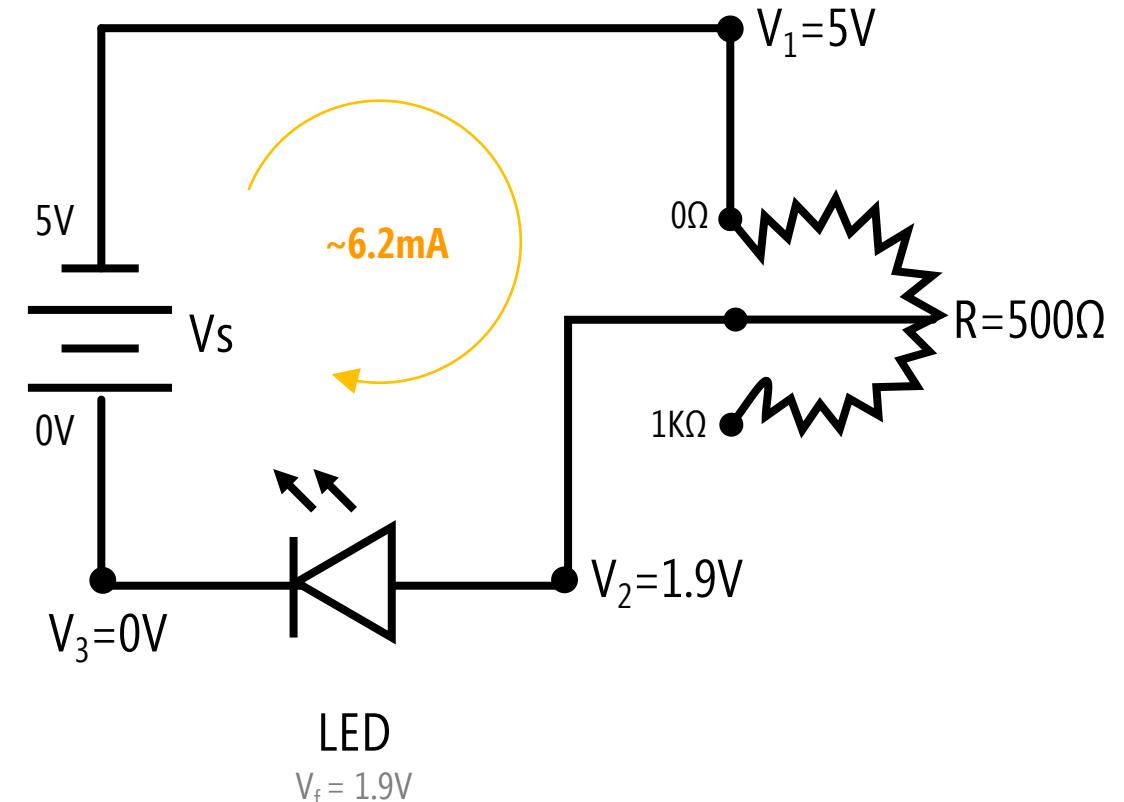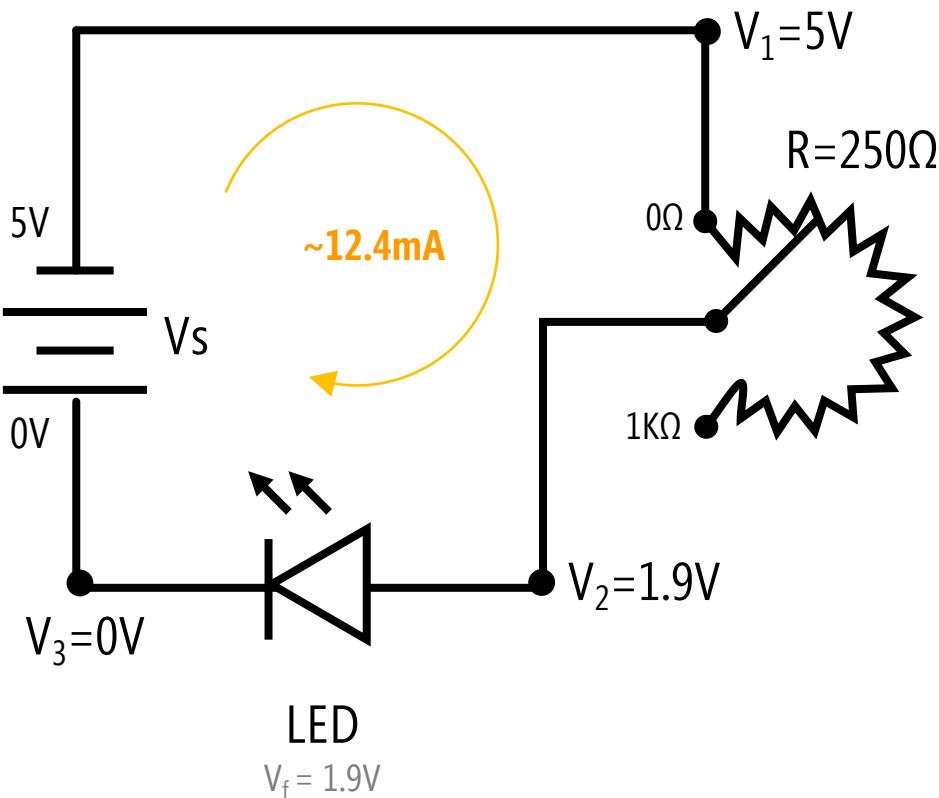



## POTENTIOMETER

# POTENTIOMETER EXAMPLES

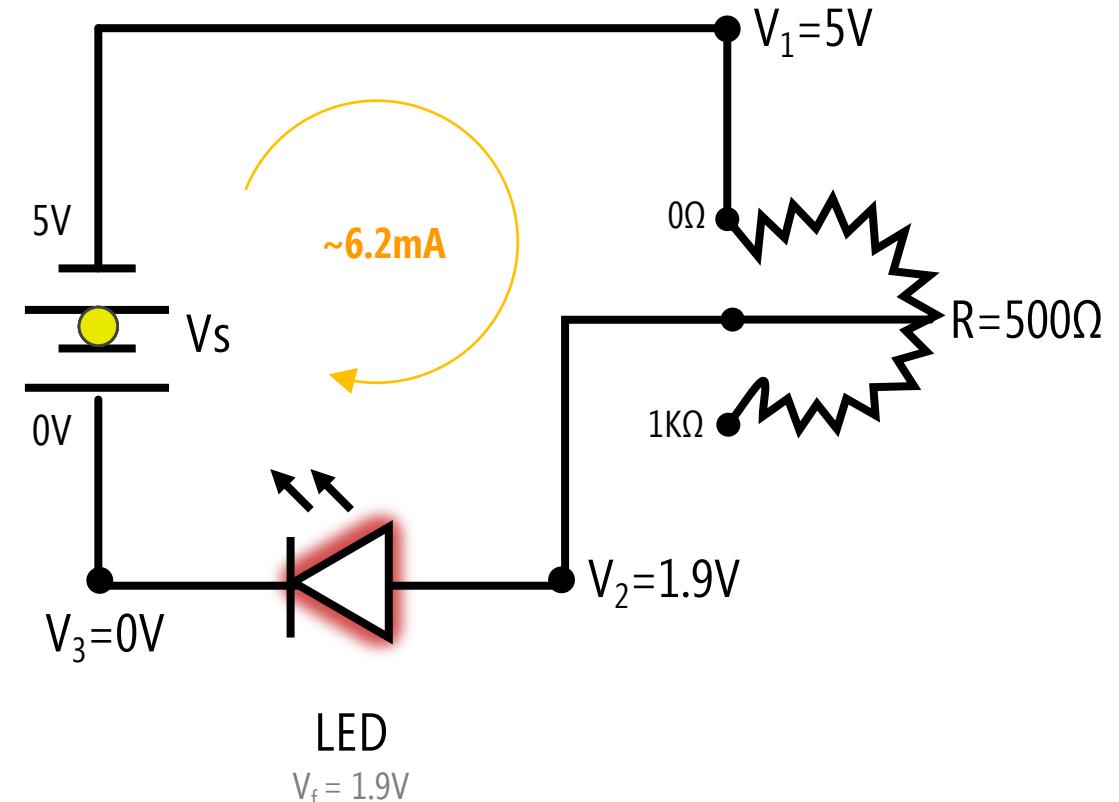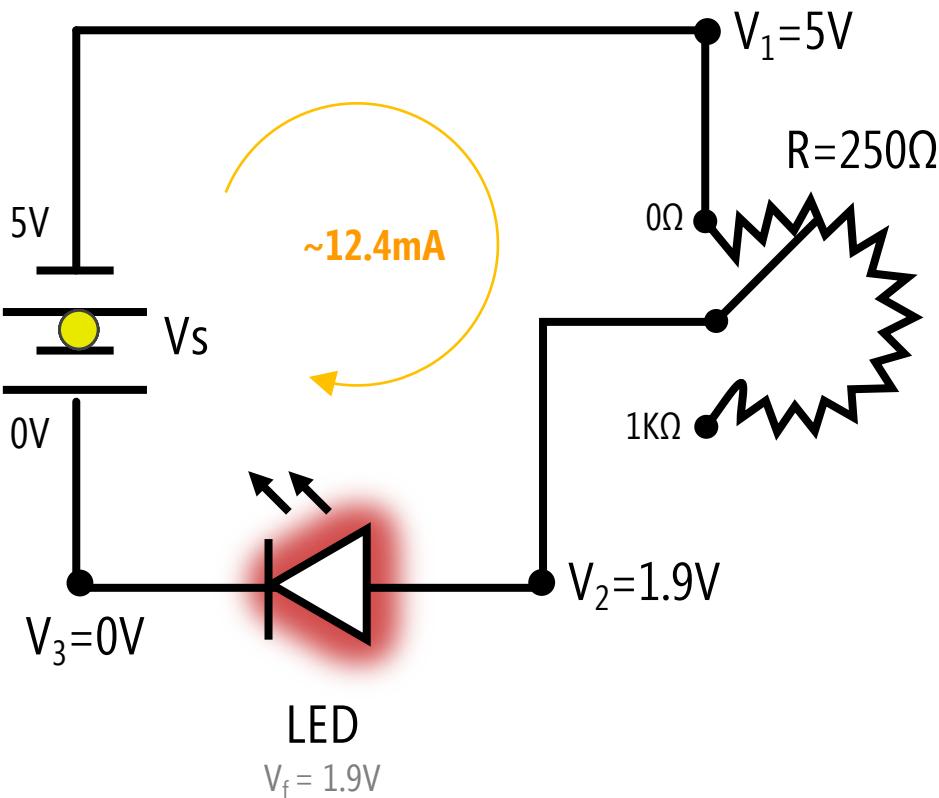

## POTENTIOMETER

# POTENTIOMETER EXAMPLES

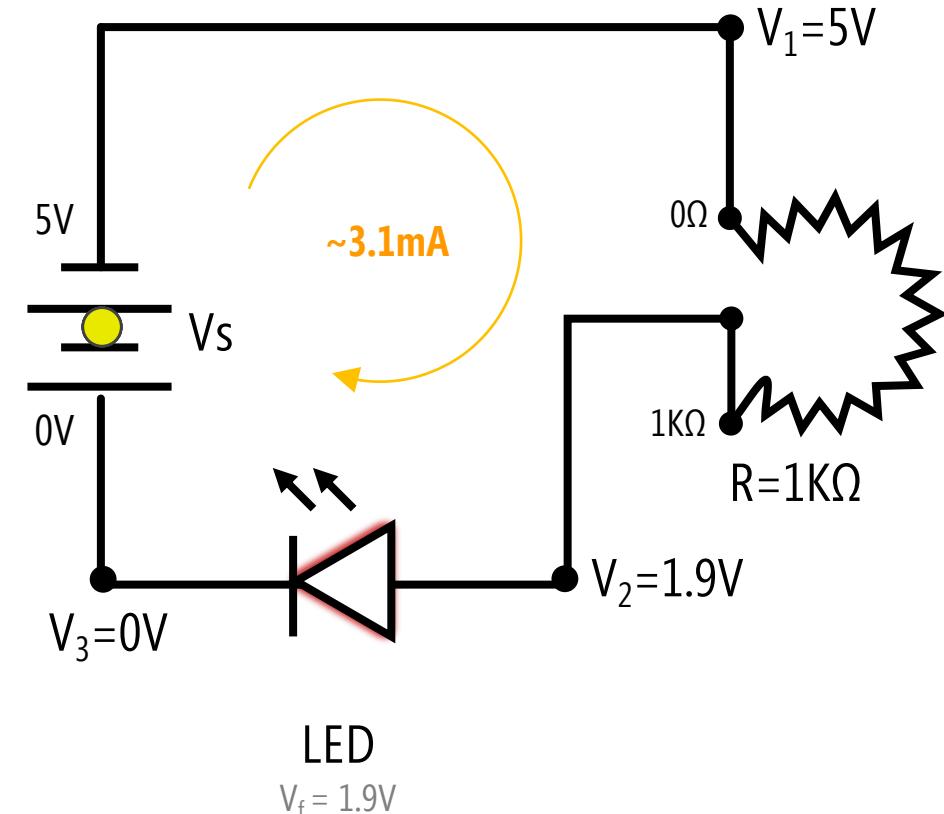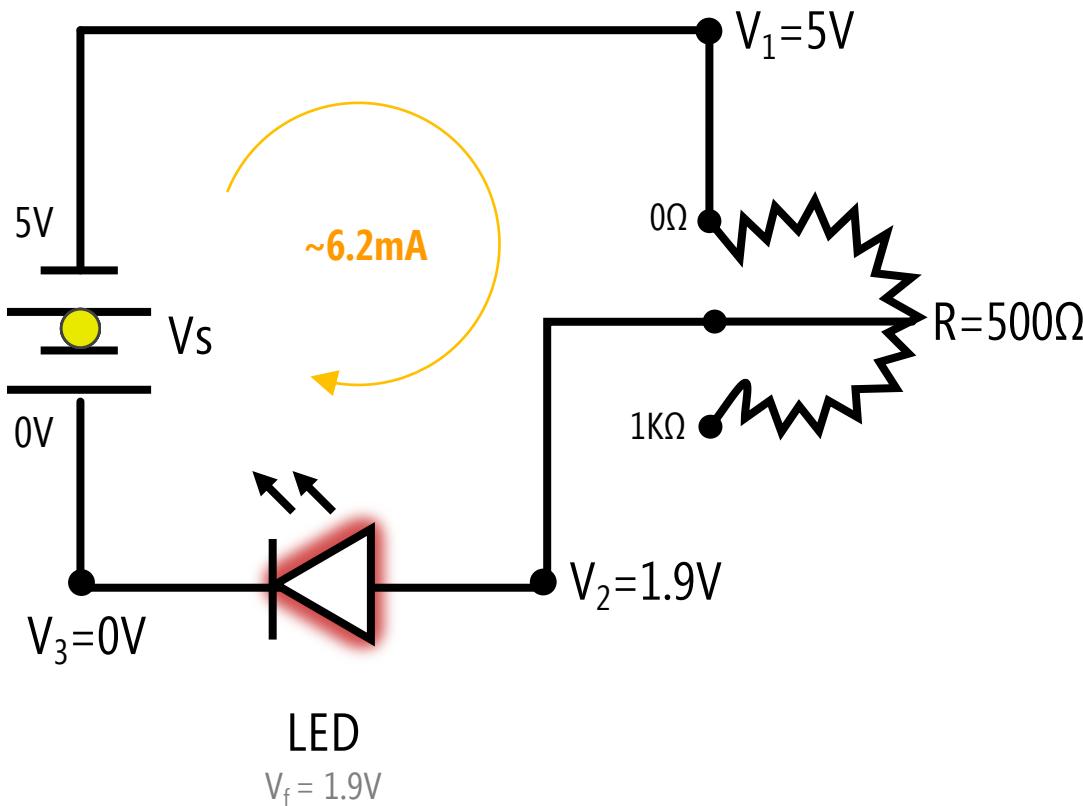

POTENTIOMETERS


# LINEAR VS. EXPONENTIAL RESISTANCE






VARIABLE RESISTORS

# BREADBOARD-FRIENDLY TRIMPOT

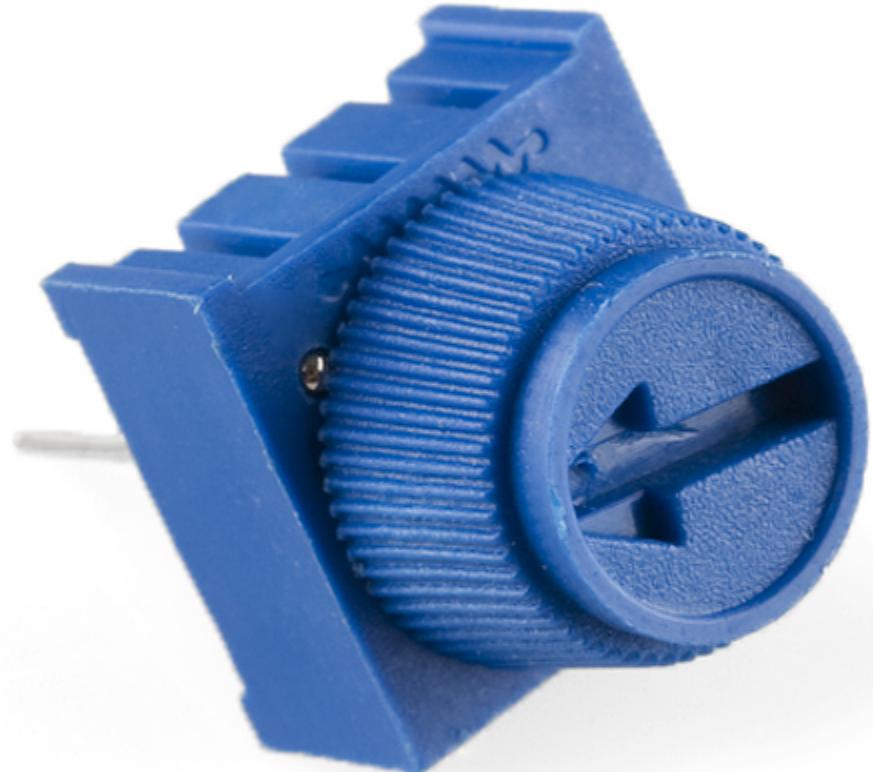


## POTENTIOMETERS
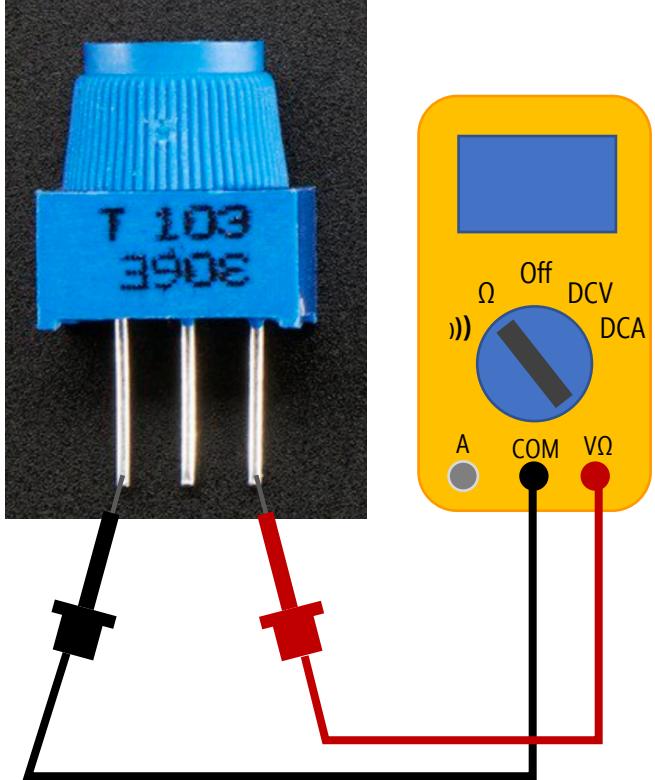
# ACTIVITY: EXPLORE THE POT WITH A MULTIMETER



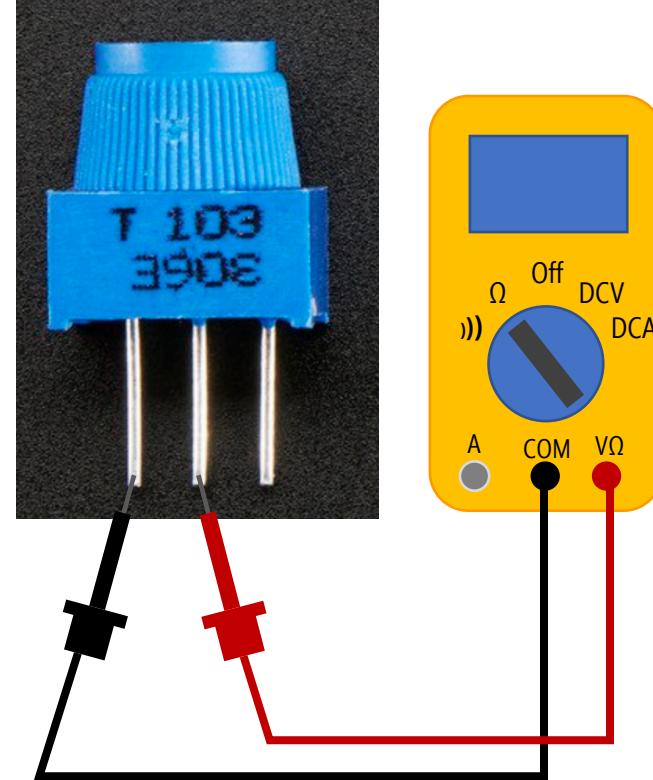
Hook up the **two outer legs** to the multimeter.  
What happens when you turn the knob?




Hook up the **middle** and an **outer leg** to the  
multimeter. What happens when you turn the knob?

## POTENTIOMETERS
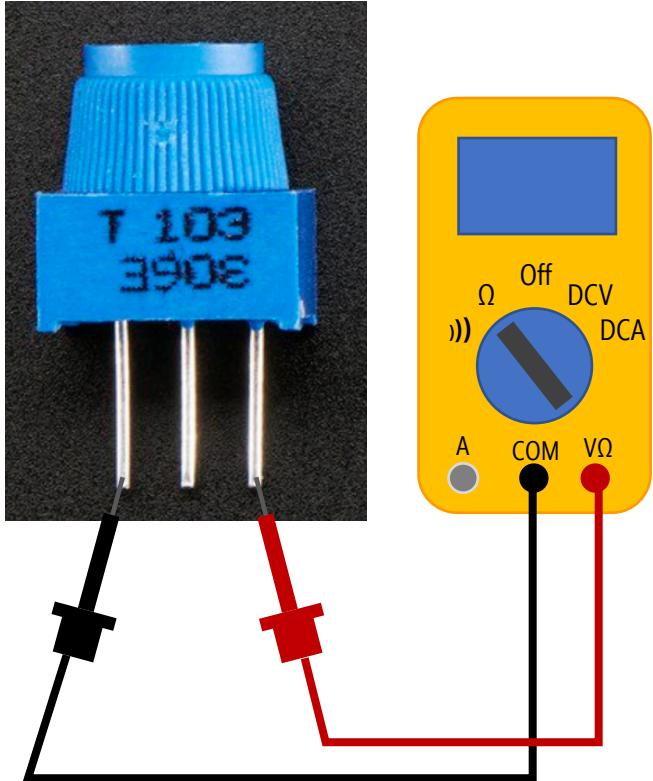
# ACTIVITY: EXPLORE THE POT WITH A MULTIMETER



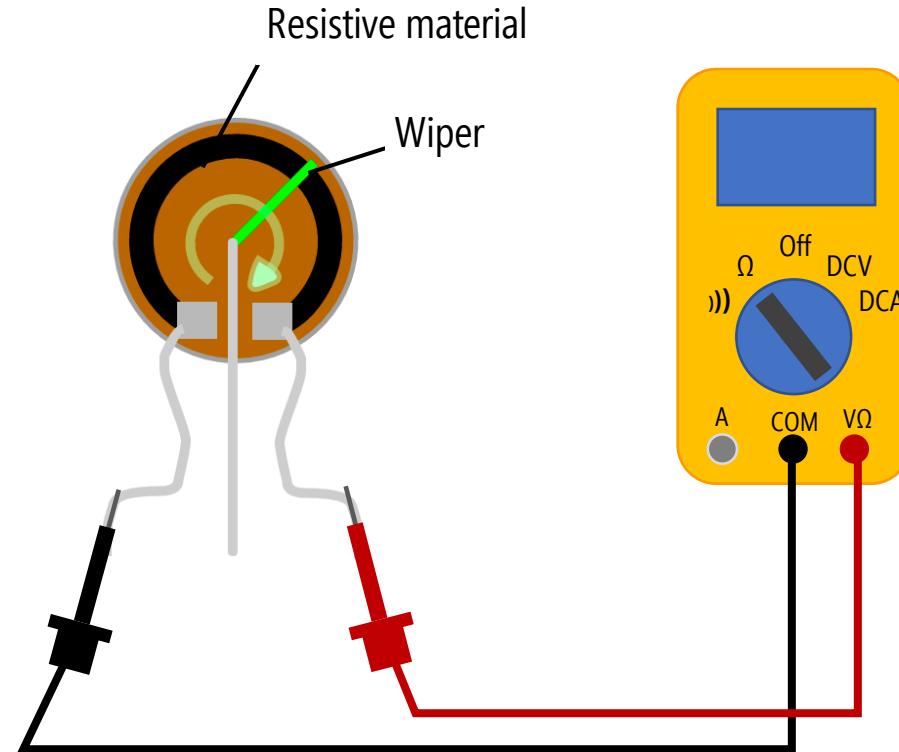
Hook up the **two outer legs** to the multimeter.  
What happens when you turn the knob?



**Answer:** Nothing! The multimeter will always read the full max resistance of the potentiometer since you are measuring

## POTENTIOMETERS

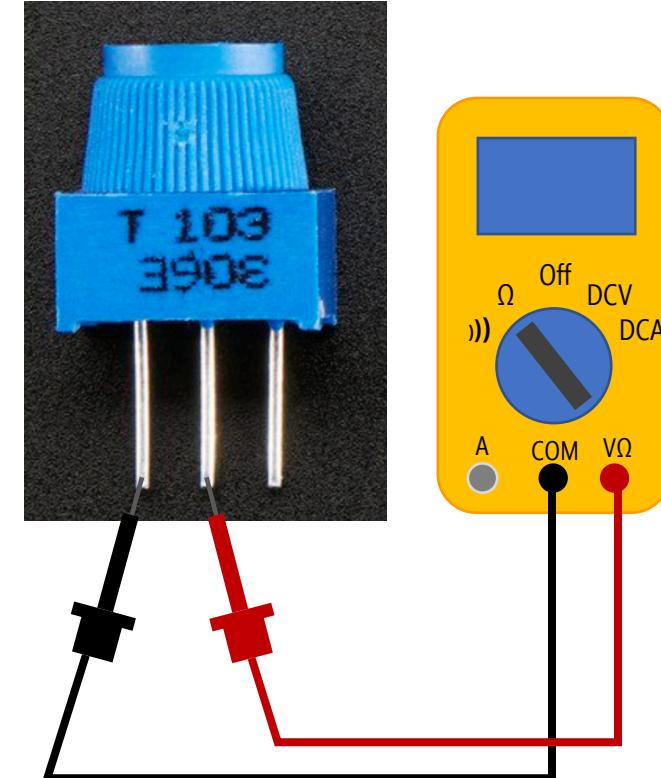
# ACTIVITY: EXPLORE THE POT WITH A MULTIMETER




Hook up the **middle** and an **outer leg** to the multimeter. What happens when you turn the knob?

## POTENTIOMETERS
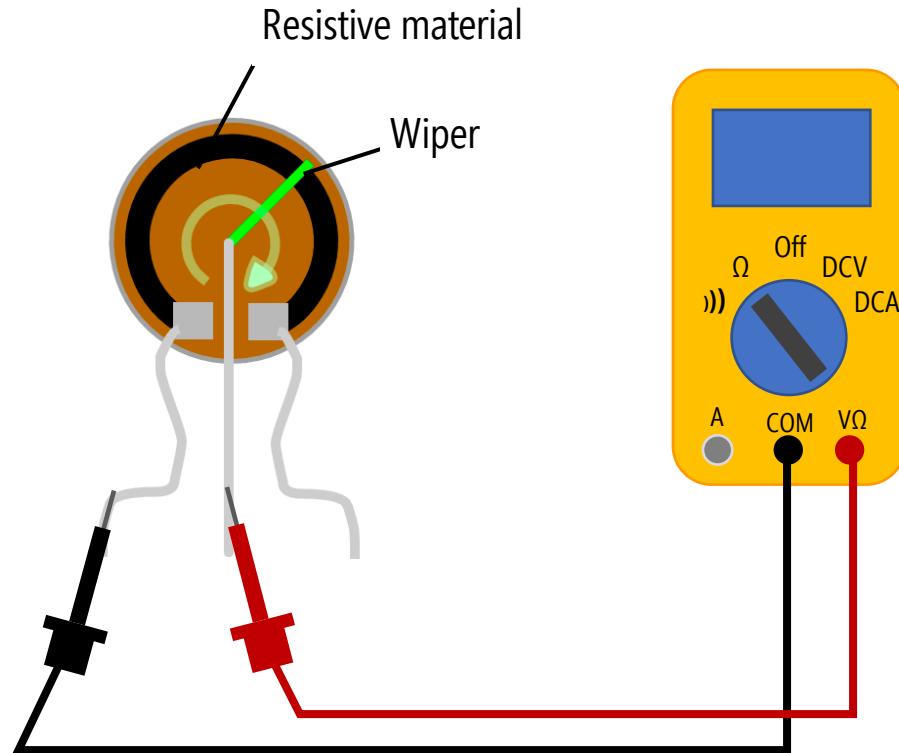
# ACTIVITY: EXPLORE THE POT WITH A MULTIMETER



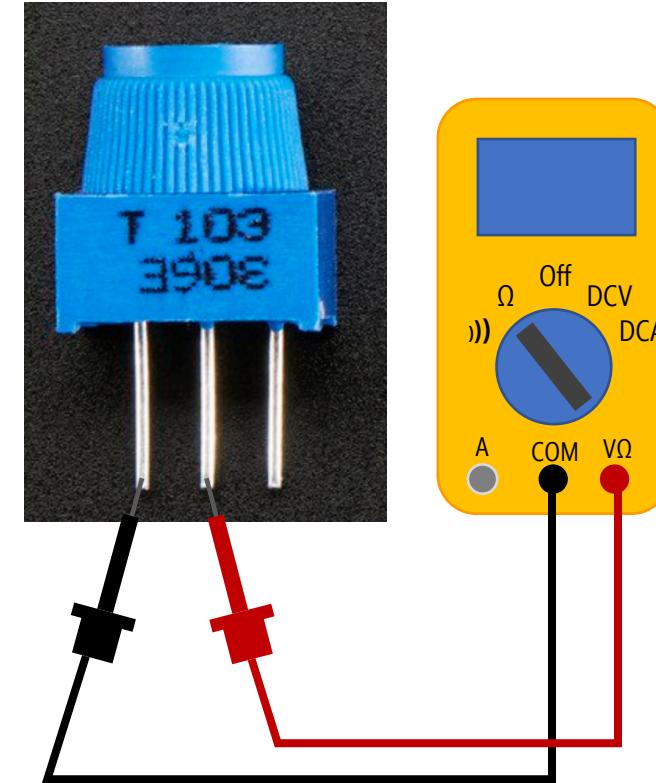
**Answer:** You'll see the resistance change based on the position of the knob. In this case,  $0\Omega$  with the knob all the way to the left,  $5K\Omega$  in middle, and  $10K\Omega$  with knob all the way to the right



Hook up the **middle** and an **outer leg** to the multimeter. What happens when you turn the knob?

VARIABLE RESISTORS
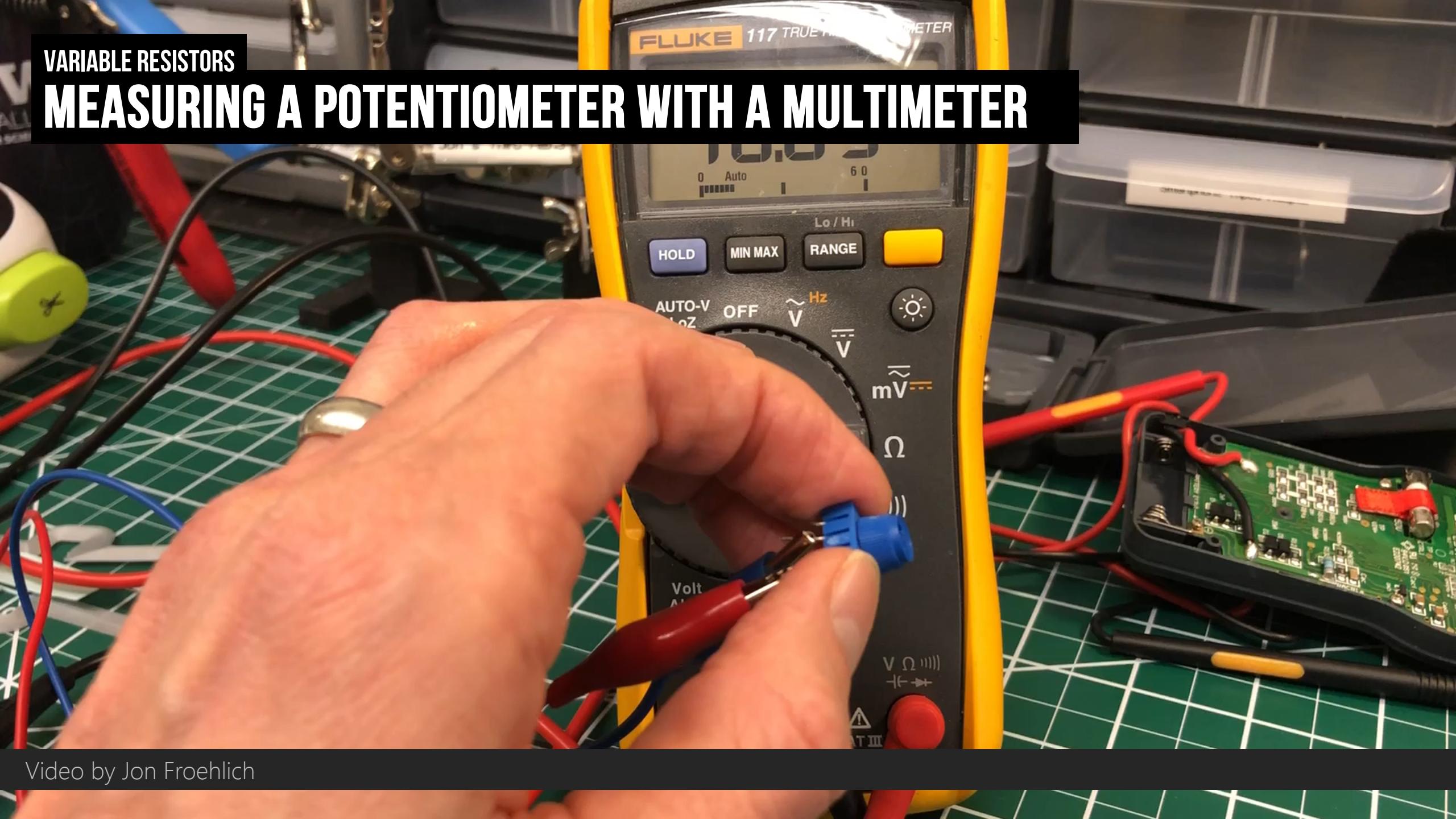
# MEASURING A POTENTIOMETER WITH A MULTIMETER



Video by Jon Froehlich

FLUKE 117 TRUE RATIO MULTIMETER

10.09

0 Auto

kΩ

HOLD

MIN MAX

RANGE

Lo / Hi

AUTO-V

OFF

Hz

Hz

V

V

mV

Hz

Ω

Ω

Ω

Ω

Ω

Ω

Ω

Ω

Ω

Ω

Ω

Volt

Alt


V Ω

Ω

Ω

Ω

Ω

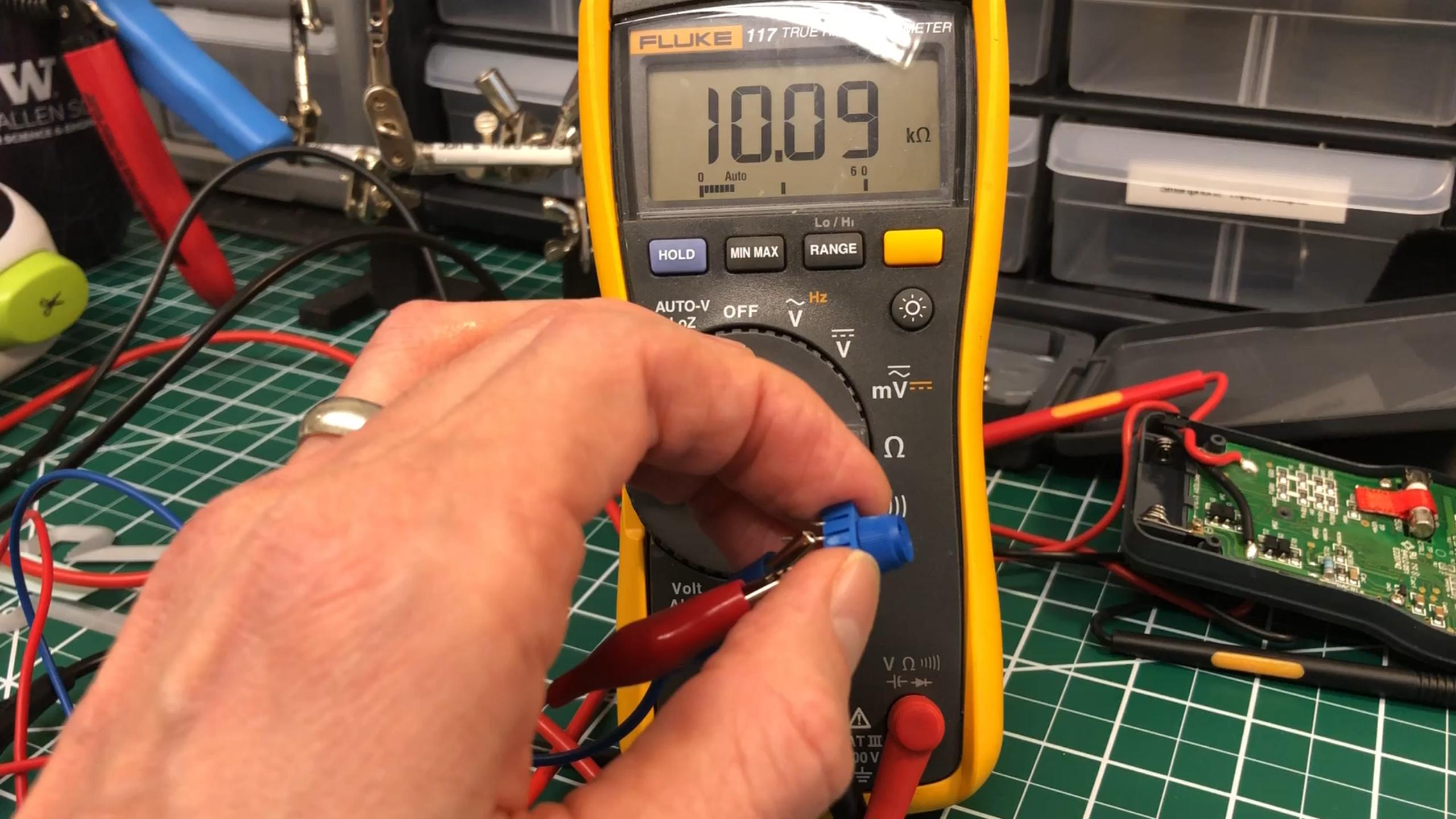


POTENTIOMETERS

# ACTIVITY HOOK UP AN LED WITH A POT & ALLIGATOR CLIPS

## POTENTIOMETERS
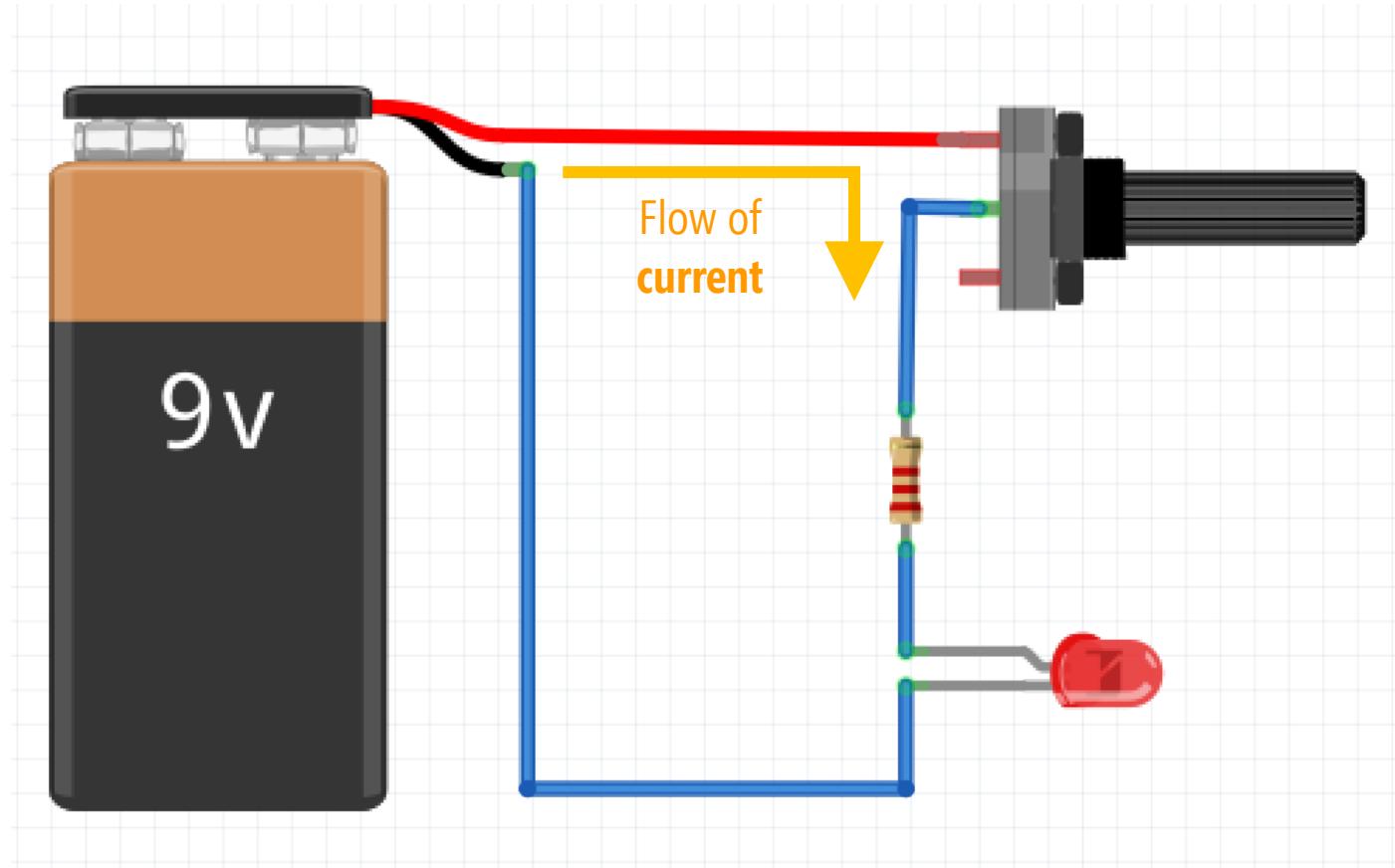
# ACTIVITY HOOK UP AN LED WITH A POT & ALLIGATOR CLIPS




ANALOG INPUT


# NOW LET'S DO THE SAME THING BUT WITH ARDUINO

Here, we will make **two separate circuits**.

One for input


One for output

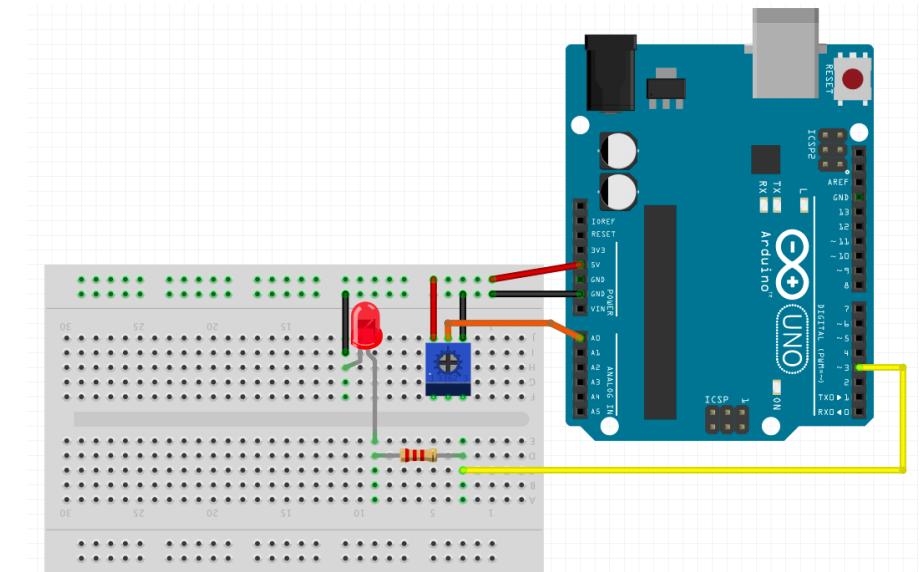

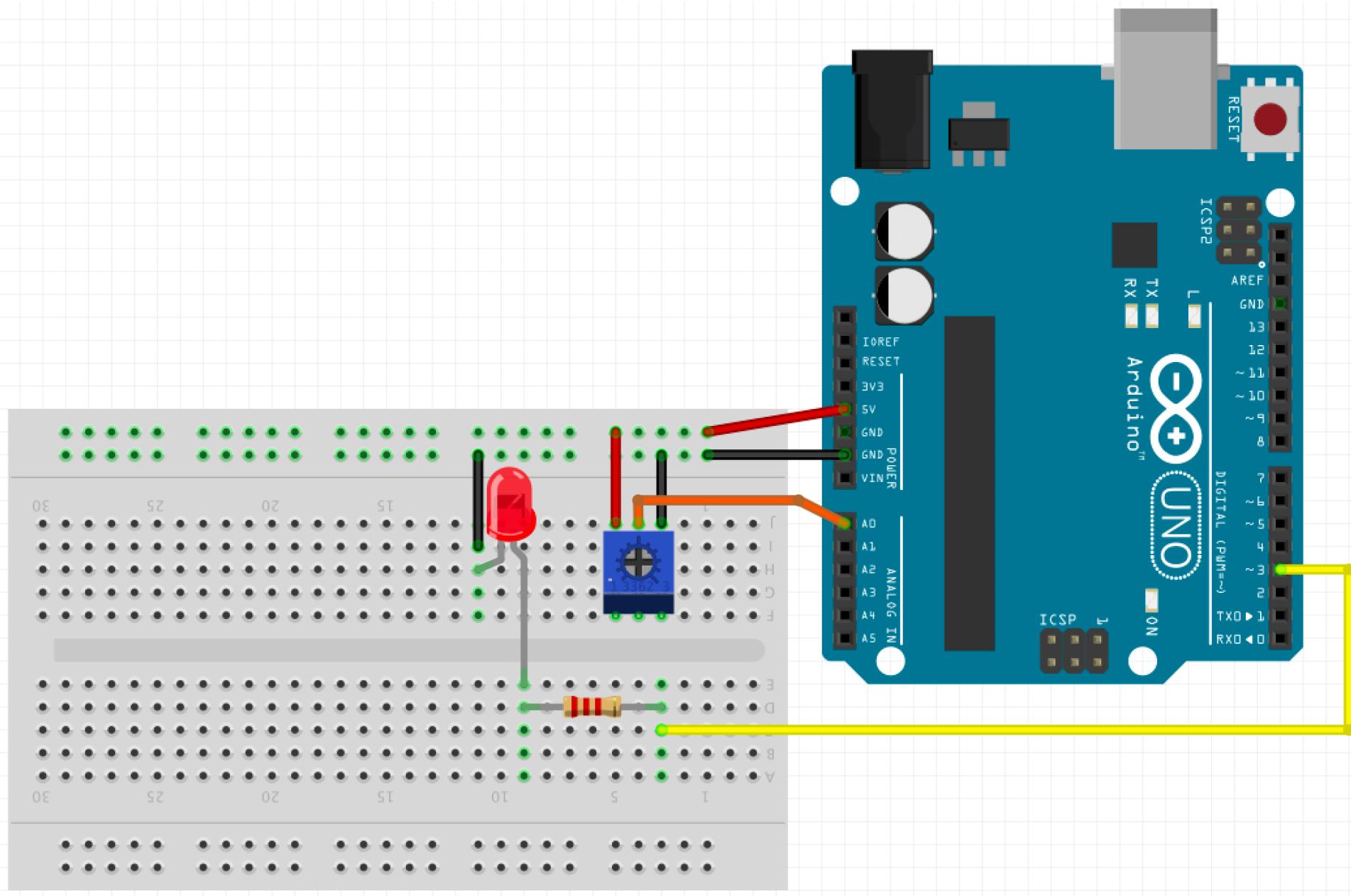

ANALOG INPUT
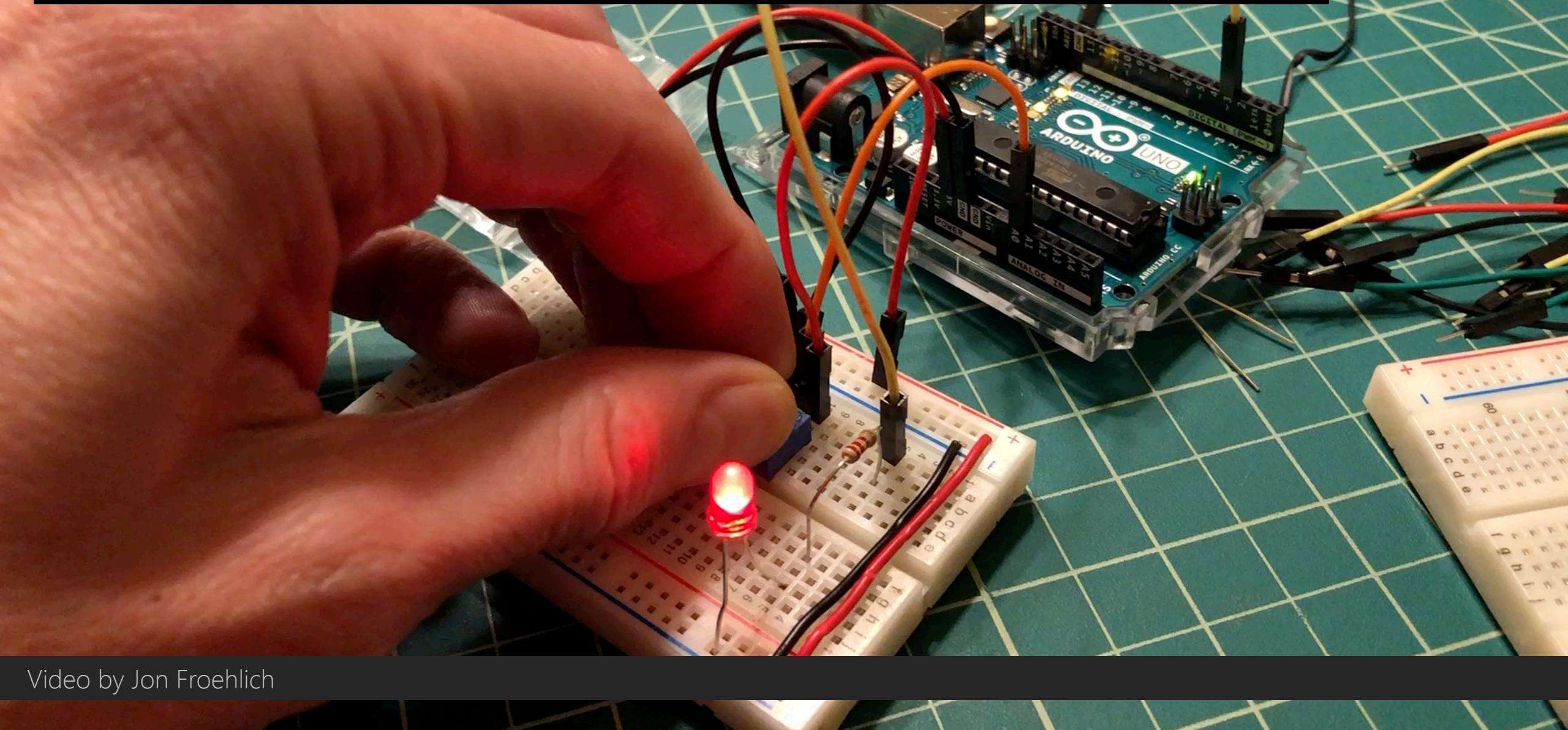
# ACTIVITY: CONTROL LED BRIGHTNESS WITH A TRIM POT




Video by Jon Froehlich

ANALOG INPUT

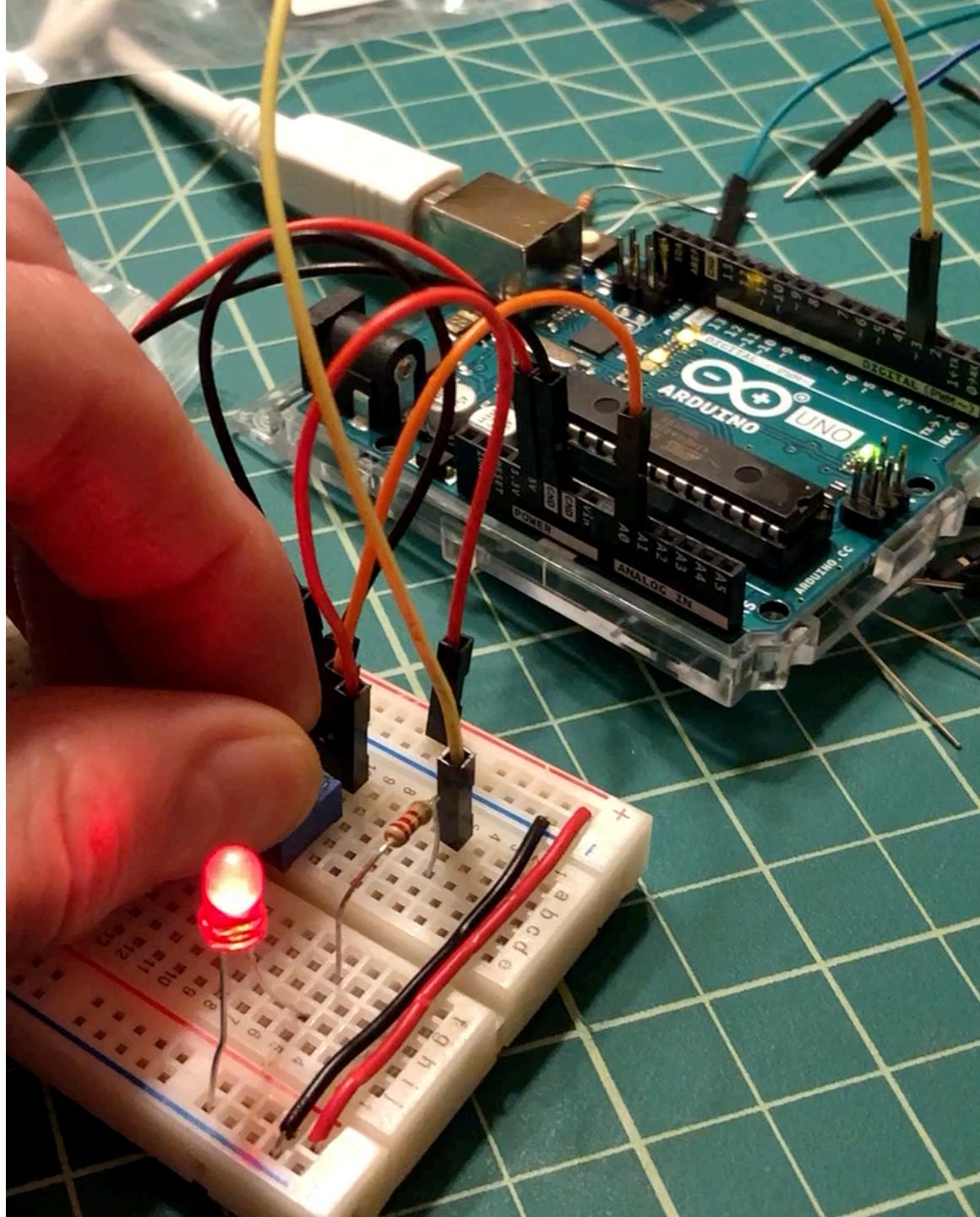
# ACTIVITY: CONTROL LED BRIGHTNESS WITH TRIMPOT

Design circuit + software to read the potentiometer value on A0 and proportionally set the brightness of an LED on Pin 3



ANALOG INPUT
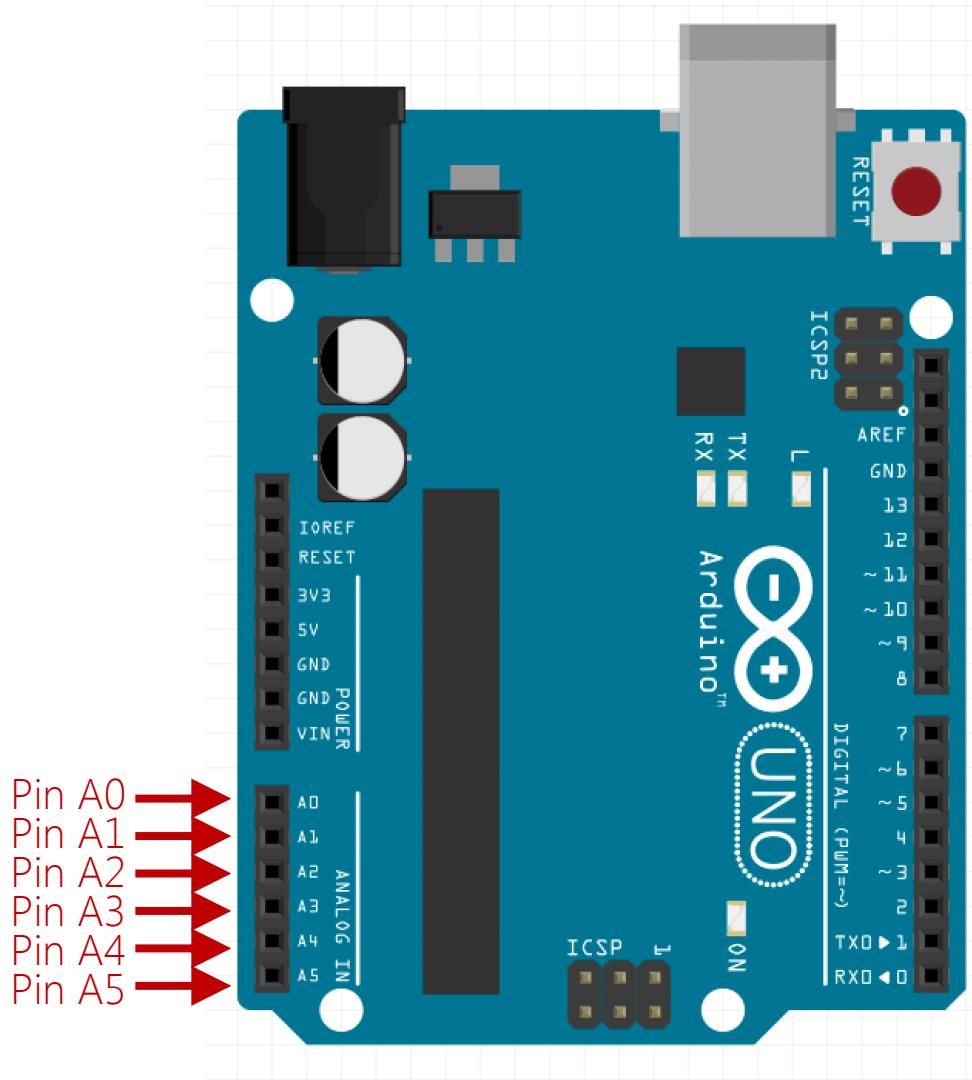
# UNO AND LEONARDO BOARDS HAVE SIX ANALOG INPUTS



## ANALOG INPUT

# int analogRead(pin)

Reads the voltage from the specified analog pin & returns an integer (0 – 1023)

## Syntax

analogRead(pin)

## Parameters

pin: the analog pin to read from

## Returns

An integer between 0 and 1023 (inclusive).

### TrimpotLED

```
// The Arduino Uno ADC is 10 bits (thus, 0 - 1023 values)
#define MAX_ANALOG_INPUT_VAL 1023

const int LED_OUTPUT_PIN = 3;
const int POT_INPUT_PIN = A0;

void setup() {
  pinMode(LED_OUTPUT_PIN, OUTPUT);
  pinMode(POT_INPUT_PIN, INPUT);
  Serial.begin(9600);
}

void loop() {
  // read the potentiometer value
  int potVal = analogRead(POT_INPUT_PIN);

  // the analogRead on the Arduino Uno goes from 0 to 1023. We need to remap
  // this value to the smaller range (0-255) since the analogWrite function can
  // only write out 0-255 (a byte--2^8). The map function provides a linear
  // mapping to do this (however, a better way would likely be some sort of
  // non-linear mapping given that perceived LED brightness is not linear with current,
  // perhaps logarithmic)
  int ledVal = map(potVal, 0, MAX_ANALOG_INPUT_VAL, 0, 255);

  // print the raw pot value and the converted led value
  Serial.print(potVal);
  Serial.print(",");
  Serial.println(ledVal);

  // write out the LED value. This value is translated to voltage by:
  // voltageVal = max_voltage * val/255 or voltageVal = 3.3V * val/255 in
  // the case of the RedBear Duo
  analogWrite(LED_OUTPUT_PIN, ledVal);

  delay(100);
}
```

## ANALOG INPUT

# int analogRead(pin)

Reads the voltage value from the specified analog pin and returns it as an integer (0 – 1023)

ATmega microcontroller uses  
a **10-bit analog-to-digital-convert** (so, input voltages  
are mapped to 0-1023)

On a Uno or Leonardo, this  
yields a **resolution of 0.0049**  
**volts** (5 volts / 1024 units)

The reading freq is about  
**~10,000Hz**

[Reference](#) > [Language](#) > [Functions](#) > [Analog io](#) > [Analogread](#)

## analogRead()

[Analog I/O]

### Description

Reads the value from the specified analog pin. Arduino boards contain a multichannel, 10-bit analog to digital converter. This means that it will map input voltages between 0 and the operating voltage(5V or 3.3V) into integer values between 0 and 1023. On an Arduino UNO, for example, this yields a resolution between readings of: 5 volts / 1024 units or, 0.0049 volts (4.9 mV) per unit. See the table below for the usable pins, operating voltage and maximum resolution for some Arduino boards.

The input range can be changed using [analogReference\(\)](#), while the resolution can be changed (only for Zero, Due and MKR boards) using [analogReadResolution\(\)](#).

On ATmega based boards (UNO, Nano, Mini, Mega), it takes about 100 microseconds (0.0001 s) to read an analog input, so the maximum reading rate is about 10,000 times a second.

## ANALOG INPUT

# int analogRead(pin)

Reads the voltage value from the specified analog pin and returns it as an integer (0 – 1023)

## Syntax

analogRead(pin)

## Parameters

pin: the analog pin to read from

## Returns

An integer between 0 and 1023 (i

## ANALOG OUTPUT analogWrite(pin, value)

Writes an analog value between 0 and 5V to a pin using pulse-width modulation (PWM).

## Syntax

analogWrite(pin, value)

## Parameters

pin: the pin to write to.

value: an integer value between 0 & 255 which roughly maps to 0 – 5V on the Arduino Uno.

<https://www.arduino.cc/reference/en/language/functions/analog-io/analogwrite/>

```
FadeOneDirection §
* Adapted from http://www.arduino.cc/en/Tutorial/Fade
*
*/
const int LED_OUTPUT_PIN = 3;
int _curBrightness = 0; // how bright the LED is
// The setup function runs once when you press reset or power the board
void setup() {
  // set the LED pin to as an output
  pinMode(LED_OUTPUT_PIN, OUTPUT);
}
// The loop function runs over and over again forever
void loop() {
  // set the brightness of the LED pin:
  analogWrite(LED_OUTPUT_PIN, _curBrightness);
  // change the brightness for next time through the loop:
  _curBrightness = _curBrightness + 1;
  // the maximum value that we can write out to analogWrite is 255
  // so check to see if the current brightness value is greater than 255
  // and if it is, reset the brightness to 0 (which is off)
  if (_curBrightness > 255){
    _curBrightness = 0;
  }
  // wait for 30 milliseconds to see the dimming effect
  delay(30);
}
```

## HELPER FUNCTION

# map(value, fromLow, fromHigh, toLow, toHigh)

Remaps a number from one range to another. Warning: it does not constrain values to be within the range.

### Syntax

```
map(value, fromLow, fromHigh, toLow, toHigh)
```

### Parameters

value: the number to map

fromLow: the lower bound of the value's current range

fromHigh: the upper bound of the value's current range

toLow: the lower bound of the value's target range

toHigh: the upper bound of the value's target range

### Returns

The mapped value

#### TrimpotLED

```
// The Arduino Uno ADC is 10 bits (thus, 0 - 1023 values)
#define MAX_ANALOG_INPUT_VAL 1023

const int LED_OUTPUT_PIN = 3;
const int POT_INPUT_PIN = A0;

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    pinMode(POT_INPUT_PIN, INPUT);
    Serial.begin(9600);
}

void loop() {

    // read the potentiometer value
    int potVal = analogRead(POT_INPUT_PIN);

    // the analogRead on the Arduino Uno goes from 0 to 1023. We need to remap
    // this value to the smaller range (0-255) since the analogWrite function can
    // only write out 0-255 (a byte--2^8). The map function provides a linear
    // mapping to do this (however, a better way would likely be some sort of
    // non-linear mapping given that perceived LED brightness is not linear with current,
    // perhaps logarithmic)
    int ledVal = map(potVal, 0, MAX_ANALOG_INPUT_VAL, 0, 255);

    // print the raw pot value and the converted led value
    Serial.print(potVal);
    Serial.print(",");
    Serial.println(ledVal);



    // write out the LED value. This value is translated to voltage by:
    // voltageVal = max_voltage * val/255 or voltageVal = 3.3V * val/255 in
    // the case of the RedBear Duo
    analogWrite(LED_OUTPUT_PIN, ledVal);

    delay(100);
}
```

## ANALOG INPUT
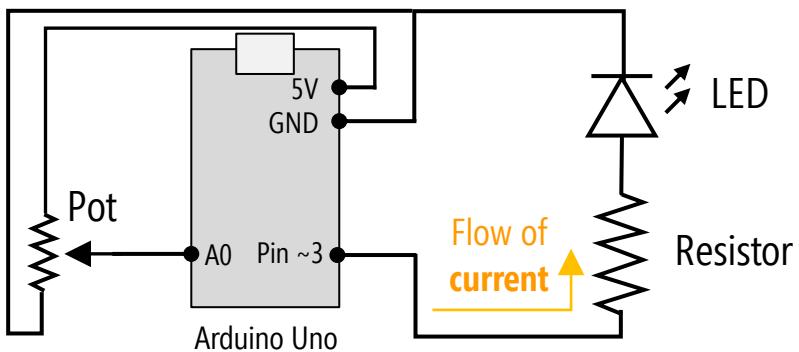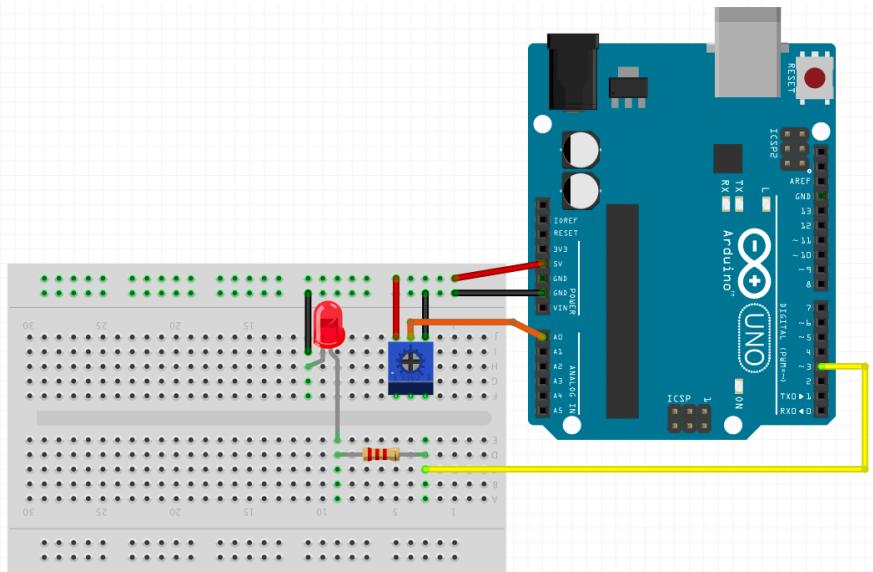
# ACTIVITY: CONTROL LED BRIGHTNESS WITH POTENTIOMETER

**Circuit:** Fade LED on/off via pot value



**Code:** Fade LED on/off via pot value

### TrimpotLED

```
// The Arduino Uno ADC is 10 bits (thus, 0 - 1023 values)
#define MAX_ANALOG_INPUT_VAL 1023

const int LED_OUTPUT_PIN = 3;
const int POT_INPUT_PIN = A0;

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    Serial.begin(9600);
}

void loop() {

    // read the potentiometer value
    int potVal = analogRead(POT_INPUT_PIN);

    // the analogRead on the Arduino Uno goes from 0 to 1023. We need to remap
    // this value to the smaller range (0-255) since the analogWrite function can
    // only write out 0-255 (a byte--2^8). The map function provides a linear
    // mapping to do this (however, a better way would likely be some sort of
    // non-linear mapping given that perceived LED brightness is not linear with current,
    // perhaps logarithmic)
    int ledVal = map(potVal, 0, MAX_ANALOG_INPUT_VAL, 0, 255);

    // print the raw pot value and the converted led value
    Serial.print(potVal);
    Serial.print(",");
    Serial.println(ledVal);

    // write out the LED value. This value is translated to voltage by:
    // voltageVal = max_voltage * val/255 or voltageVal = 3.3V * val/255 in
    // the case of the RedBear Duo
    analogWrite(LED_OUTPUT_PIN, ledVal);

    delay(100);
}
```

## TrimpotLED

```
// The Arduino Uno ADC is 10 bits (thus, 0 - 1023 values)
#define MAX_ANALOG_INPUT_VAL 1023

const int LED_OUTPUT_PIN = 3;
const int POT_INPUT_PIN = A0;

void setup() {
    pinMode(LED_OUTPUT_PIN, OUTPUT);
    Serial.begin(9600);
}

void loop() {

    // read the potentiometer value
    int potVal = analogRead(POT_INPUT_PIN);

    // the analogRead on the Arduino Uno goes from 0 to 1023. We need to remap
    // this value to the smaller range (0-255) since the analogWrite function can
    // only write out 0-255 (a byte--2^8). The map function provides a linear
    // mapping to do this (however, a better way would likely be some sort of
    // non-linear mapping given that perceived LED brightness is not linear with current,
    // perhaps logarithmic)
    int ledVal = map(potVal, 0, MAX_ANALOG_INPUT_VAL, 0, 255);

    // print the raw pot value and the converted led value
    Serial.print(potVal);
    Serial.print(",");
    Serial.println(ledVal);

    // write out the LED value. This value is translated to voltage by:
    // voltageVal = max_voltage * val/255 or voltageVal = 3.3V * val/255 in
    // the case of the RedBear Duo
    analogWrite(LED_OUTPUT_PIN, ledVal);

    delay(100);
}
```

# int analogRead() : Tips/Warnings

If the analog **input pin is not connected** to anything, the value returned by `analogRead()` will fluctuate based on a number of factors (*e.g.*, the values of the other analog inputs, how close your hand is to the board, *etc.*). Try it! ☺

# int analogRead() : Tips/Warnings


If the analog **input pin is not connected** to anything, the value returned by analogRead() will fluctuate based on a number of factors (*e.g.*, the values of the other analog inputs, how close your hand is to the board, *etc.*). Try it! ☺

If you **execute multiple, consecutive** analogReads() **across different pins**, you might get noisy values. Instead:

- add a couple of ms delay between measurements on different pins
- perform two analogRead() on the same pin, dump the 1st & keep the 2nd

ANALOG INPUT



# HOW DOES THIS WORK?

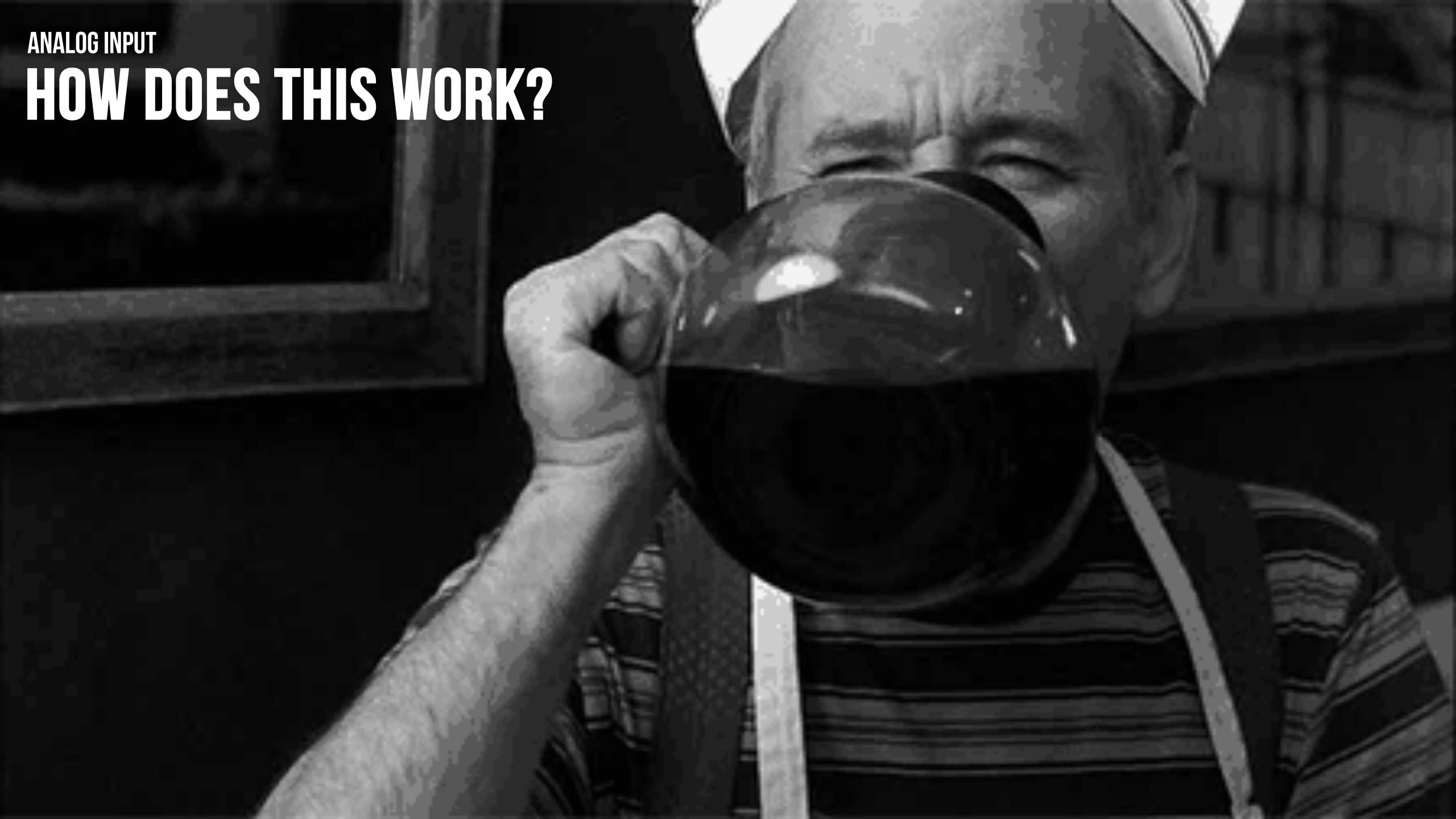


ANALOG INPUT
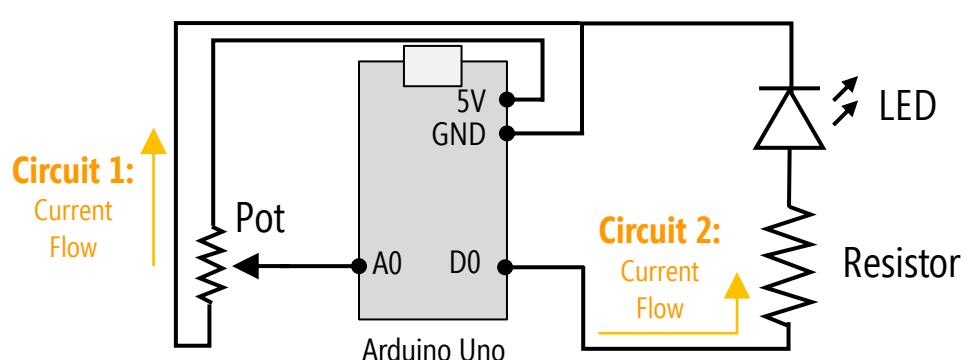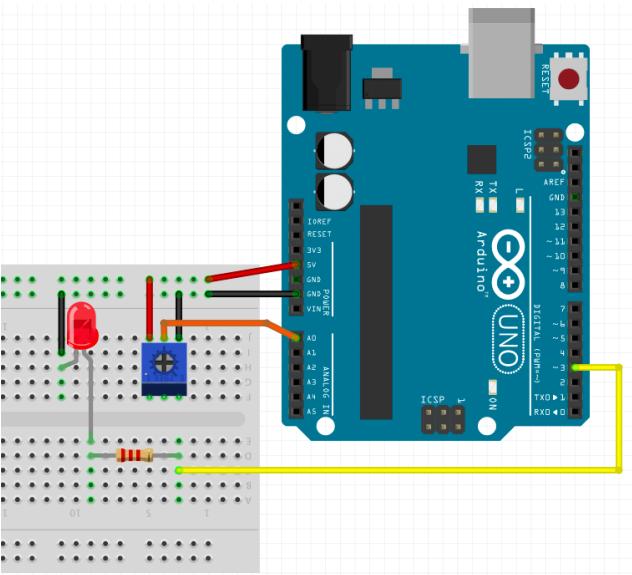
# HOW DOES THIS WORK?

Let's redraw our circuit into an equivalent but simpler representation



Schematic Representation 1


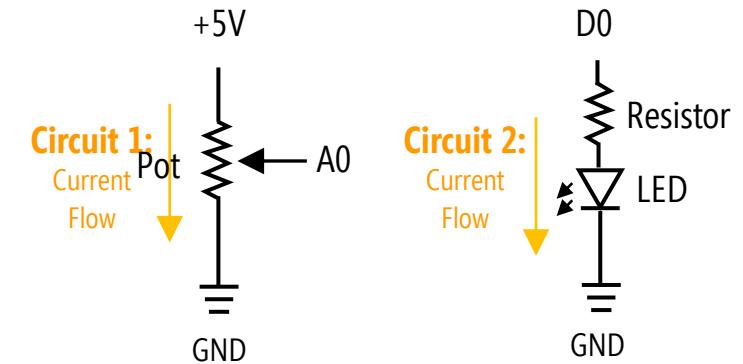


Schematic Representation 2


ANALOG INPUT
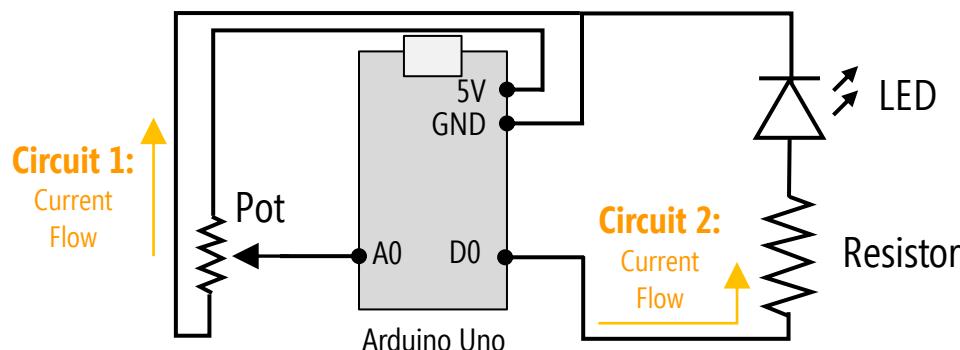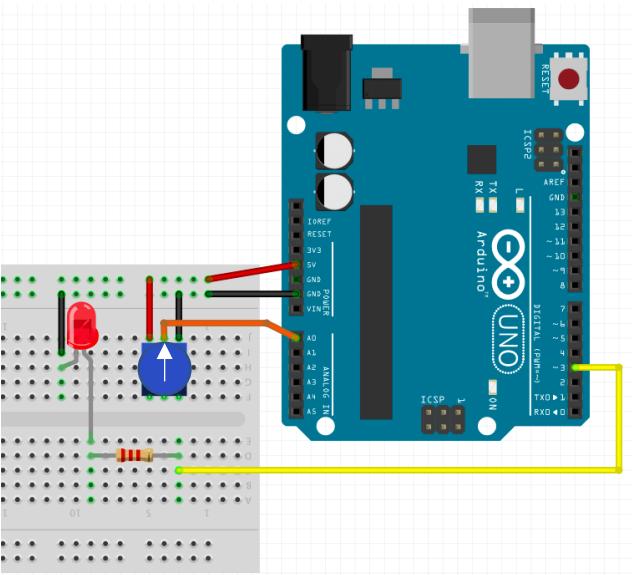
# HOW DOES THIS WORK?

Let's redraw our circuit into an equivalent but simpler representation





Schematic Representation 1

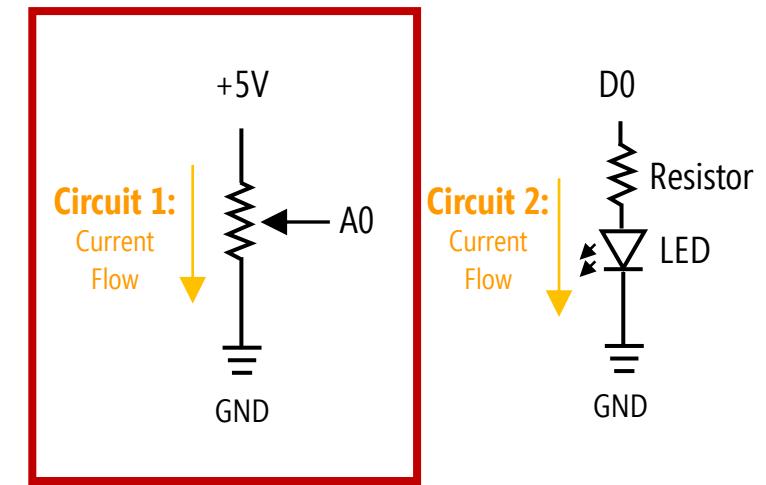

Schematic Representation 2
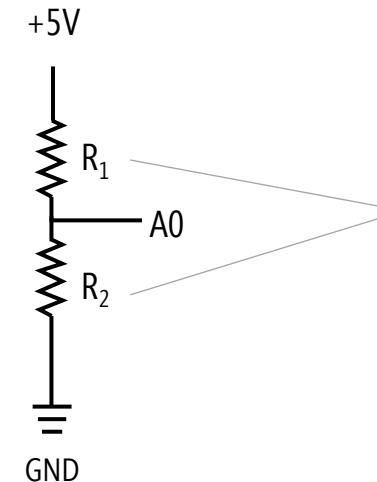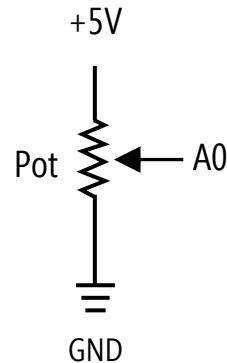
# HOW DOES THIS WORK?


Another way to think about the potentiometer



$R_1$  and  $R_2$  change based on knob position (but always sum to same value. So, for a  $10K\Omega$  pot,  $R_1 + R_2 = 10K\Omega$ )


ANALOG INPUT
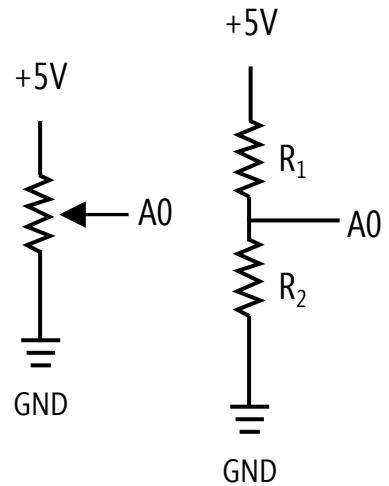
# WHAT IF THE POT IS SET TO $5\text{K}\Omega$ ?



# WHAT IF THE POT IS SET TO 5KΩ?

What is  $V_{A0}$  equal to?

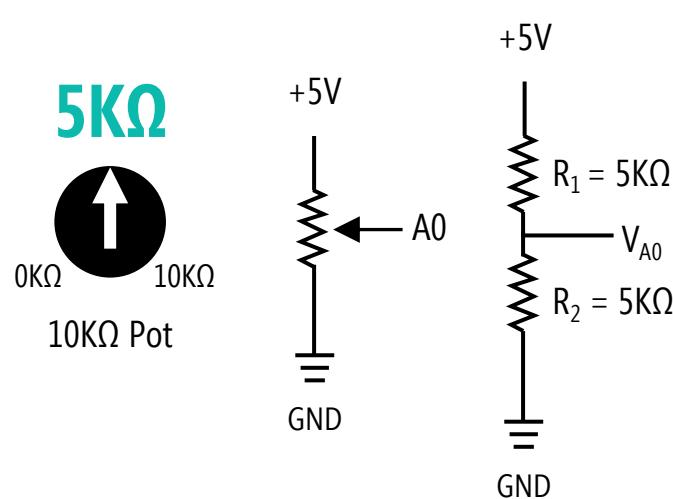

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{5,000\Omega + 5,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 5,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 2.5V$$

# WHAT IF THE POT IS SET TO 5KΩ?

**5KΩ**  
  
 0KΩ 10KΩ  
 10KΩ Pot

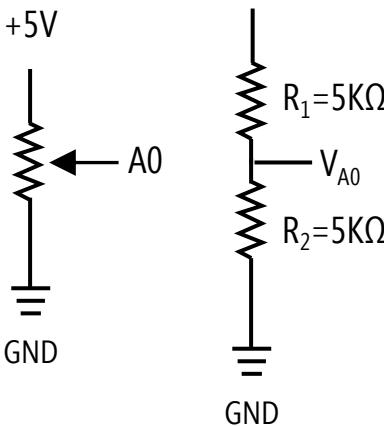

What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{5,000\Omega + 5,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 5,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 2.5V \quad \text{analogRead(A0) would return 512}$$

# WHAT IF THE POT IS SET TO 5KΩ?

**5KΩ**  
  
 0KΩ 10KΩ  
 10KΩ Pot

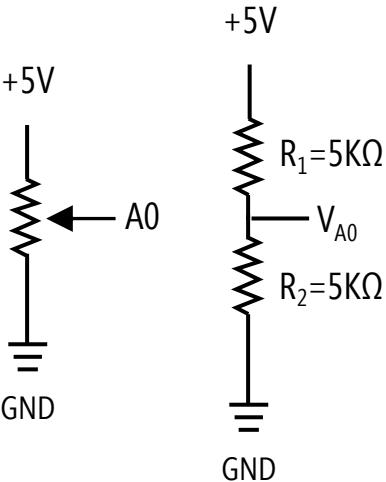

What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{5,000\Omega + 5,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 5,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 2.5V \quad \text{analogRead(A0) would return 512}$$

Why? Recall that the minimum and maximum analogRead values are 0 and 1023 respectively on the Uno. Thus:


$$\frac{2.5V}{5V} = \frac{x}{1023}$$

$$0.5 = \frac{x}{1023}$$

$$x = 0.5 * 1023 = 511.5$$

# WHAT IF THE POT IS SET TO 2KΩ?

**2KΩ**  
  
 0KΩ 10KΩ  
 10KΩ Pot

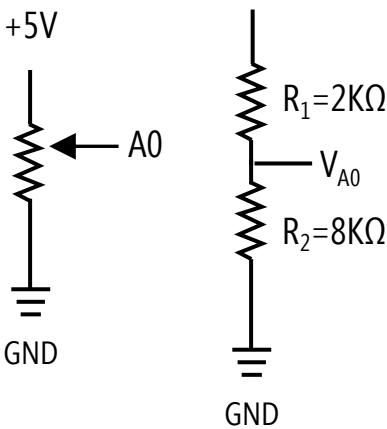

What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{2,000\Omega + 8,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 2,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 4V$$

# WHAT IF THE POT IS SET TO 2KΩ?

**2KΩ**  
  
 0KΩ 10KΩ  
 10KΩ Pot

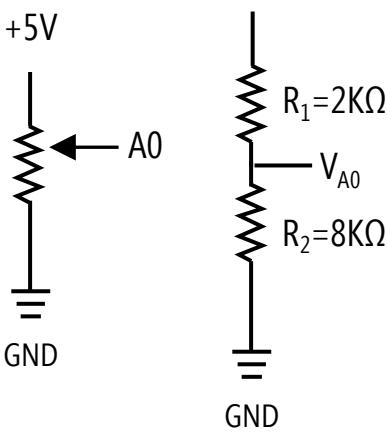

What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{2,000\Omega + 8,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 2,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 4V \quad \text{analogRead(A0) would return 818}$$

# WHAT IF THE POT IS SET TO 2KΩ?

**2KΩ**  
  
 0KΩ 10KΩ  
 10KΩ Pot

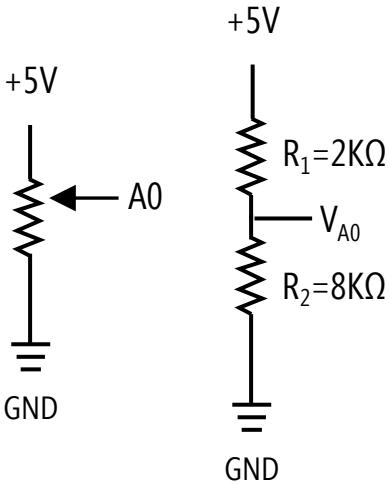

What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{2,000\Omega + 8,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\frac{4V}{5V} = \frac{x}{1023}$$

$$0.8 = \frac{x}{1023}$$


$$x = 0.8 * 1023 = 818.4$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 2,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 4V \quad \text{analogRead(A0) would return } \mathbf{818}$$
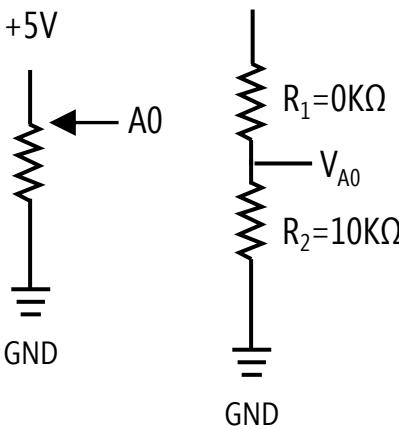
# WHAT IF THE POT IS SET TO $0\text{K}\Omega$

**$0\text{K}\Omega$**   
  
 $10\text{K}\Omega$  Pot



What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{2,000\Omega + 8,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 0\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 5V \quad \text{analogRead(A0) would return 1023}$$

## ANALOG INPUT

# WHAT IF THE POT IS SET TO 10KΩ

**10KΩ**  
0KΩ 10KΩ  
10KΩ Pot

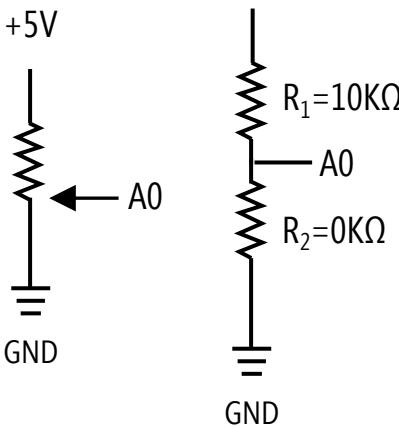

What is A0 equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{2,000\Omega + 8,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 10,000\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 0V \quad \text{analogRead(A0) would return 0}$$

# WHAT IF THE POT IS SET TO 8.2KΩ

**8.2KΩ**  
  
 0KΩ 10KΩ  
 10KΩ Pot

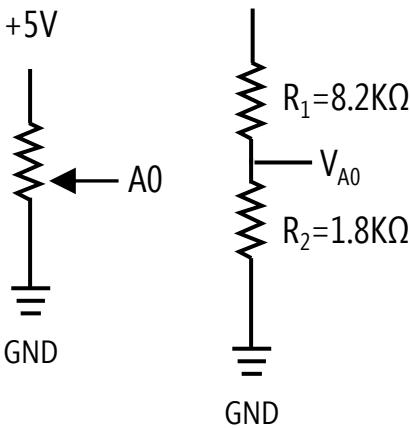

What is  $V_{A0}$  equal to?

$$\text{Current} = I = \frac{V_{\text{high potential}} - V_{\text{low potential}}}{R}$$

$$\text{Current} = I = \frac{5V - 0V}{2,000\Omega + 8,000\Omega}$$

$$\text{Current} = I = 0.0005A = 0.5mA$$

$$\text{Voltage} = V = I * R$$

$$\text{Voltage}_{A0} = V_{A0} = 5V - V_{R1}$$


$$\text{Voltage}_{A0} = V_{A0} = 5V - (0.0005A * 8,200\Omega)$$

$$\text{Voltage}_{A0} = V_{A0} = 0.9V \quad \text{analogRead(A0) would return 184}$$


## ANALOG INPUT

# LET'S LOOK AT SOME VALUES ALL TOGETHER


**0KΩ**

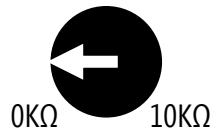


10KΩ Pot

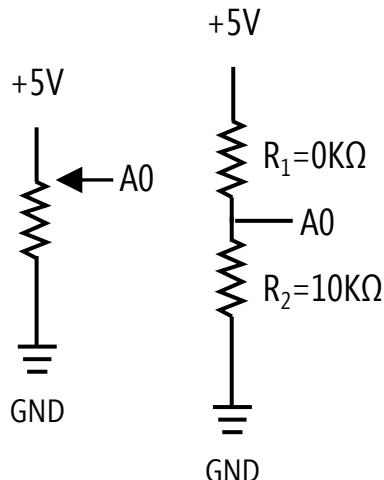


**2.8KΩ**

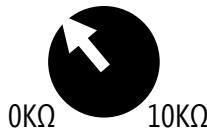


10KΩ Pot

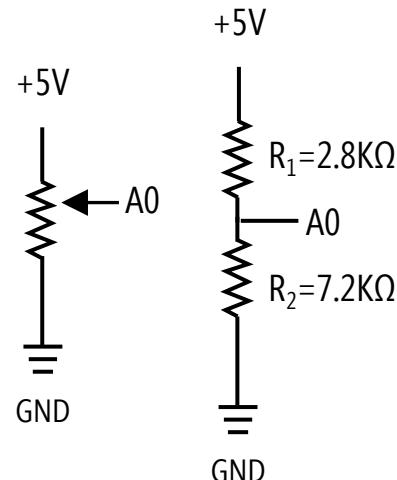

**5KΩ**

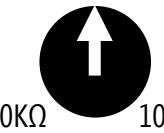


10KΩ Pot

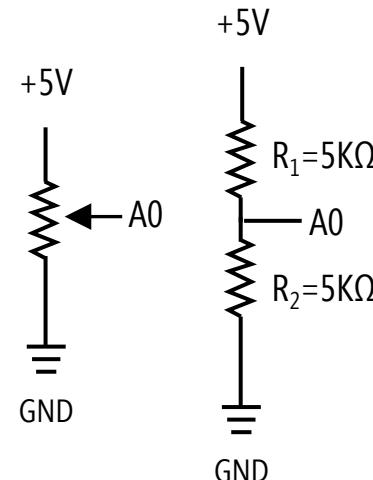


**8.4KΩ**




10KΩ Pot

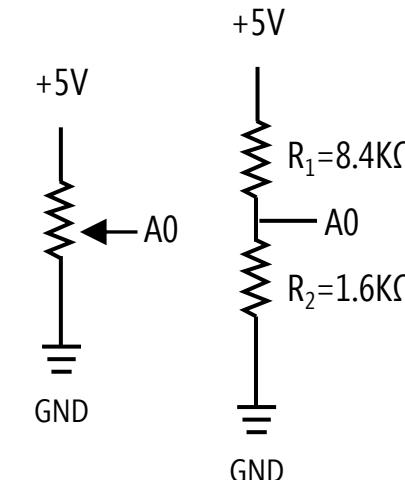

**10KΩ**

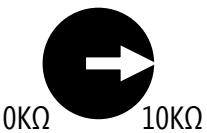

10KΩ Pot

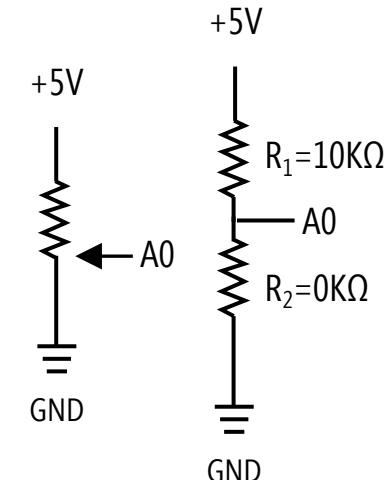

$Voltage_{A0} = V_{A0} = 5V$   
analogRead(A0) returns 1023

$Voltage_{A0} = V_{A0} = 3.6V$   
analogRead(A0) returns 737

$Voltage_{A0} = V_{A0} = 2.5V$   
analogRead(A0) returns 512


$Voltage_{A0} = V_{A0} = 0.8V$   
analogRead(A0) returns 164

$Voltage_{A0} = V_{A0} = 0V$   
analogRead(A0) returns 0


## ANALOG INPUT

# LET'S LOOK AT SOME VALUES ALL TOGETHER

**0KΩ**

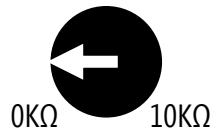


10KΩ Pot

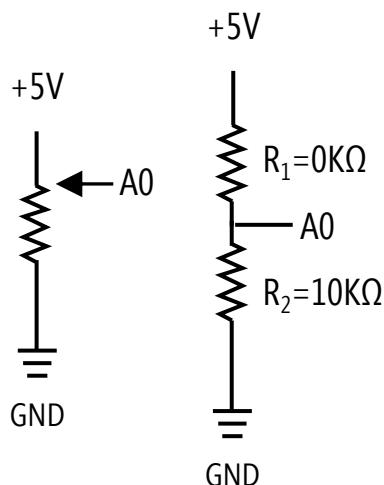


$Voltage_{A0} = V_{A0} = 5V$   
analogRead(A0) returns 1023

**2.8KΩ**

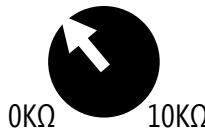


10KΩ Pot

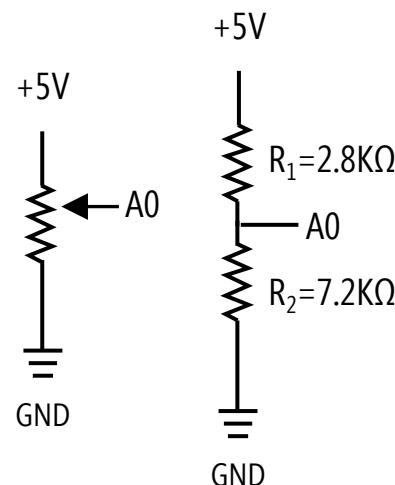


$Voltage_{A0} = V_{A0} = 3.6V$   
analogRead(A0) returns 737

**5KΩ**

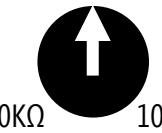


10KΩ Pot

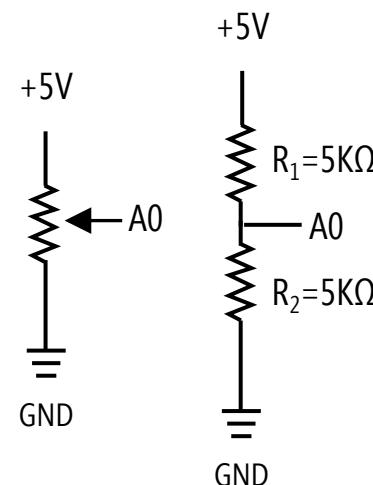


$Voltage_{A0} = V_{A0} = 2.5V$   
analogRead(A0) returns 512

**8.4KΩ**

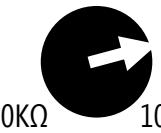


10KΩ Pot

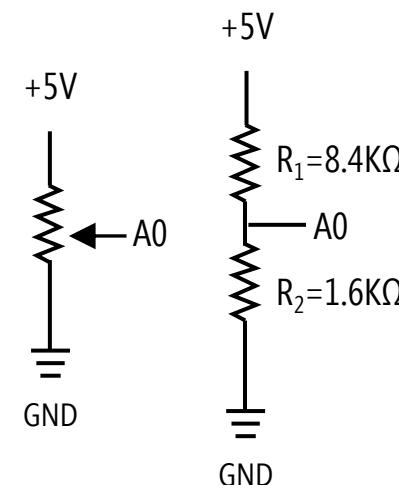


$Voltage_{A0} = V_{A0} = 0.8V$   
analogRead(A0) returns 164

**10KΩ**

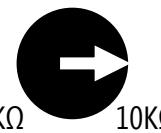

10KΩ Pot

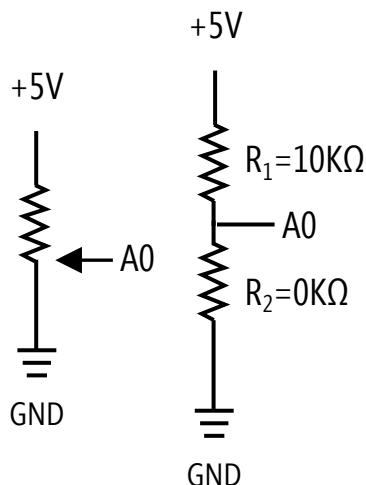






$Voltage_{A0} = V_{A0} = 0V$   
analogRead(A0) returns 0

As  $R_1$  grows big with respect to  $R_2$ ,  $V_{A0}$  drops to zero

## ANALOG INPUT
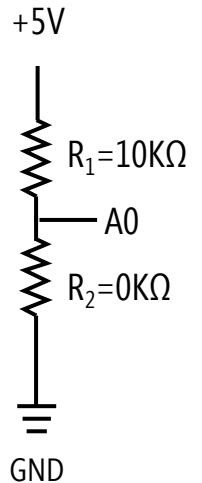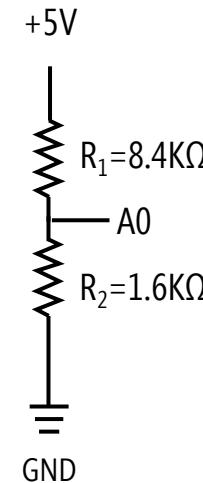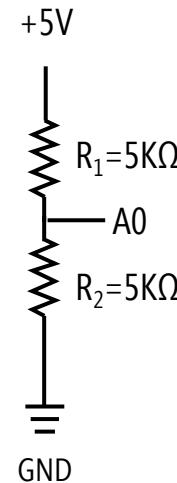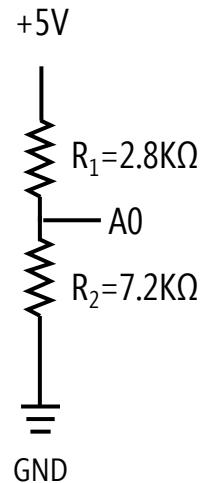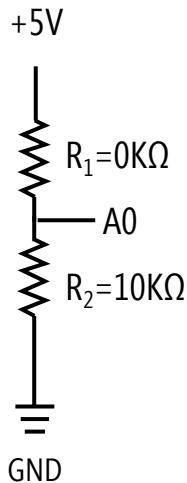
# THIS TYPE OF CIRCUIT IS CALLED A “VOLTAGE DIVIDER”

It's called a voltage divider because the voltage drops are divided across two resistors. A voltage divider is one of the primary ways that we configure our circuits to read sensor data with Arduino.



$$Voltage_{A0} = V_{A0} = 5V$$

analogRead(A0) returns 1023

$$Voltage_{A0} = V_{A0} = 3.6V$$

analogRead(A0) returns 737

$$Voltage_{A0} = V_{A0} = 2.5V$$

analogRead(A0) returns 512


$$Voltage_{A0} = V_{A0} = 0.8V$$

analogRead(A0) returns 164

$$Voltage_{A0} = V_{A0} = 0V$$

analogRead(A0) returns 0

# VOLTAGE DIVIDER EQUATION

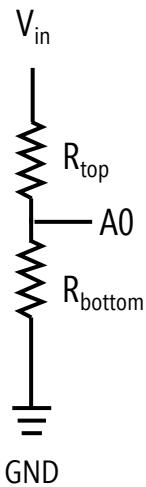

$$Voltage_{A0} = V_{A0} = V_{in} * \frac{R_{bottom}}{(R_{top} + R_{bottom})}$$

}


Note that it's the **ratio** between the two resistors that's important.

As  $R_{bottom}$  grows large with respect to  $R_{top}$ ,  $V_{A0}$  grows proportionally large

Similarly, as  $R_{top}$  grows large with respect to  $R_{bottom}$ ,  $V_{A0}$  grows proportionally small

# VOLTAGE DIVIDER EQUATION


We covered this in our  
1st Physical Computing  
Lecture

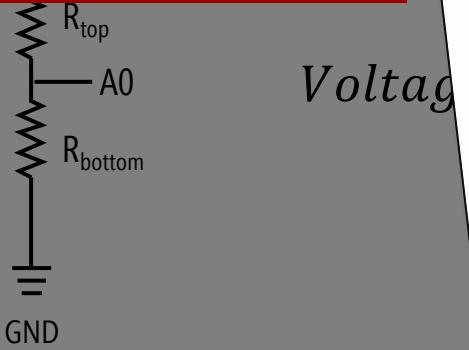

SERIES VS. PARALLEL RESISTANCE

## OHM'S LAW EXERCISE: SOLVE FOR V1, V2, AND V3

How did I know V1 and V3?

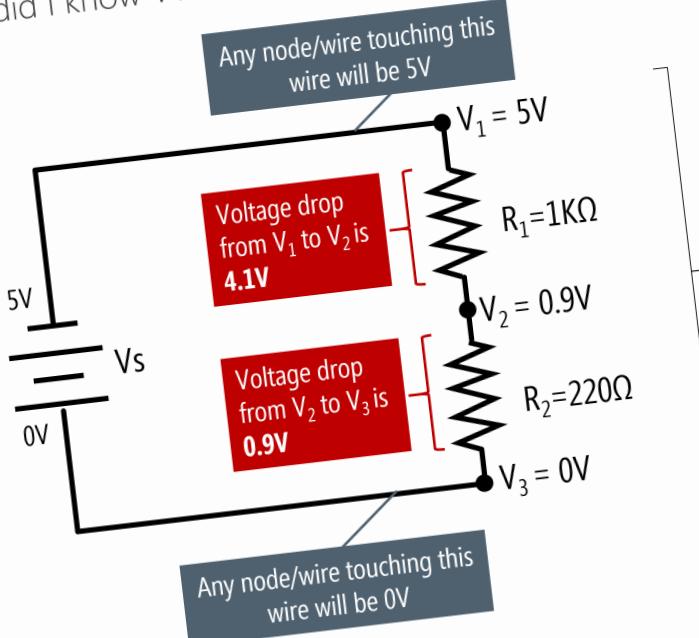


This basic circuit is called a **voltage divider** because it "splits" or "divides" voltages across nodes.

It is one of the **most common** (and useful) circuit configurations when working with microcontrollers

respect to  $R_{bottom}$ ,  $V_{A0}$  grows proportionally small

## ANALOG INPUT
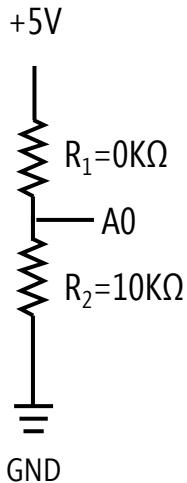
# APPLYING THE “VOLTAGE DIVIDER” EQUATION




$$V_{A0} = V_{in} * \frac{R_{bottom}}{(R_{top} + R_{bottom})}$$

$$V_{A0} = 5V * \frac{10,000\Omega}{(0\Omega + 10,000\Omega)}$$

$$V_{A0} = 5V * 1$$

$$V_{A0} = \mathbf{5V}$$

`analogRead(A0)` returns **1023**

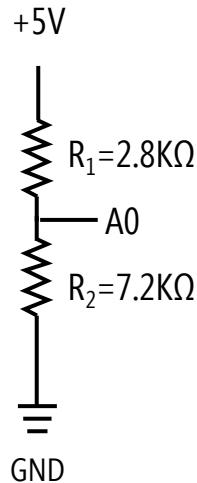


$$V_{A0} = V_{in} * \frac{R_{bottom}}{(R_{top} + R_{bottom})}$$

$$V_{A0} = 5V * \frac{7,200\Omega}{(2,800\Omega + 7,200\Omega)}$$

$$V_{A0} = 5V * 0.72$$

$$V_{A0} = \mathbf{3.6V}$$

`analogRead(A0)` returns **737**

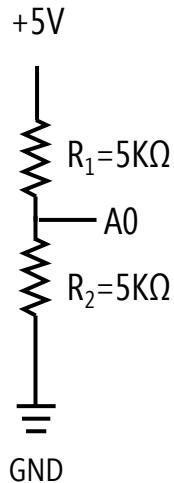


$$V_{A0} = V_{in} * \frac{R_{bottom}}{(R_{top} + R_{bottom})}$$

$$V_{A0} = 5V * \frac{5,000\Omega}{(5,000\Omega + 5,000\Omega)}$$

$$V_{A0} = 5V * 0.5$$

$$V_{A0} = \mathbf{2.5V}$$

`analogRead(A0)` returns **512**

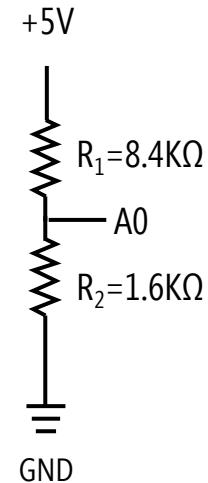


$$V_{A0} = V_{in} * \frac{R_{bottom}}{(R_{top} + R_{bottom})}$$

$$V_{A0} = 5V * \frac{1,600\Omega}{(8,400\Omega + 1,600\Omega)}$$

$$V_{A0} = 5V * 0.16$$

$$V_{A0} = \mathbf{0.8V}$$

`analogRead(A0)` returns **164**

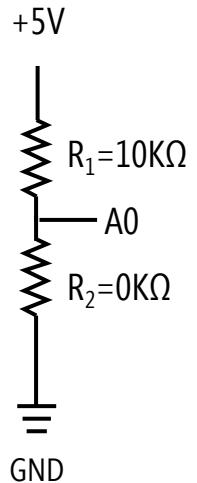

$$V_{A0} = V_{in} * \frac{R_{bottom}}{(R_{top} + R_{bottom})}$$

$$V_{A0} = 5V * \frac{0\Omega}{(10,000\Omega + 0\Omega)}$$

$$V_{A0} = 5V * 0$$

$$V_{A0} = \mathbf{0V}$$

`analogRead(A0)` returns **0**



ENORCTE.COM

## VARIABLE RESISTORS

# LOTS OF DIFFERENT KINDS OF VARIABLE RESISTORS



Potentiometer 10k; \$0.95\*



Touch Membrane Potentiometer; \$12.95



Photocell (aka photodetector or photo resistor); \$1.50



Thermistor 10k; \$0.75



Force Resistive Sensor 0.5"; \$6.95



Flex Sensor 4.5"; \$12.95